

# Combinational Logic Design Process

---

- 1. Understand the Problem**
  - what is the circuit supposed to do?
  - write down inputs (data, control) and outputs
  - draw block diagram or other picture
- 2. Formulate the Problem in terms of a truth table or other suitable design representation**
  - truth table, Boolean algebra, etc.
- 3. Choose Implementation Target**
  - PAL, PLA, Mux, Decoder, Discrete Gates
- 4. Follow Implementation Procedure**
  - K-maps, Boolean algebra

# Process Line Control Example

---

## Statement of the Problem

Rods of varying length ( $\pm 10\%$ ) travel on conveyor belt  
Mechanical arm pushes rods within spec ( $\pm 5\%$ ) to one side  
Second arm pushes rods too long to other side  
Rods too short stay on belt

3 light barriers (light source + photocell) as sensors

Design combinational logic to activate the arms

## Understanding the Problem

Inputs are three sensors, outputs are two arm control signals


Assume sensor reads "1" when tripped, "0" otherwise

Call sensors A, B, C

Draw a picture!

## Process Line Control Example (cont.)

---

 


Where to place the light sensors A, B, and C to distinguish among the three cases?

Assume that A detects the leading edge of the rod on the conveyor

# Process Line Control Example (cont.)

---

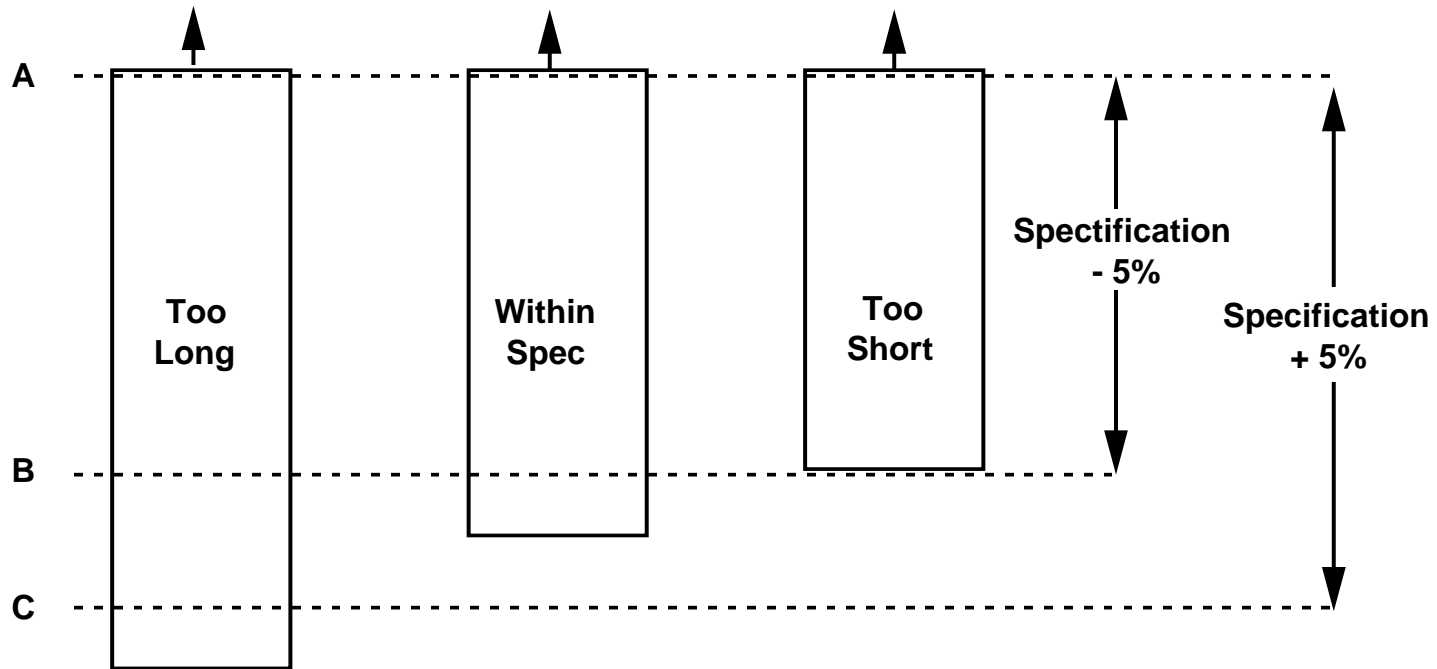

**A to B distance place apart at specification - 5%**

**A to C distance placed apart at specification +5%**

## Process Line Control Example (cont.)


---

A	B	C	Meaning	Accept	Long
0	0	0	No bar	0/x	0/x
0	0	1	Rod arriving	0	0
0	1	0	?	0	0
0	1	1	Arriving	0	0
1	0	0	Too short	0	0
1	0	1	?	0	0
1	1	0	just right	1	0
1	1	1	long	0	1

$$\text{Accept} = ABC\bar{C}$$

$$\text{Long} = ABC$$

# Combinational vs. Sequential Logic

 


Network implemented from logic gates.  
The presence of feedback distinguishes between **sequential** and **combinational** networks.
 
## **Combinational logic**




no feedback among inputs and outputs  
outputs are a pure function of the inputs  
e.g., seat belt light:

(Dbelt, Pbelt, Passenger) mapped into (Light)


   
# Circuit Timing Behavior



Simple model: gates react after fixed delay


  
# Hazards/Glitches



Circuit can temporarily go to incorrect states



Must filter out temporary states



# Safe Sequential Circuits

---

Clocked elements on feedback, perhaps outputs

Clock signal synchronizes operation

Clocked elements hide glitches/hazards

