

111

*Single Cycle CPU*


ENGR 3410 - Computer Architecture

Mark L. Chang

Fall 2006

# Datapath & Control

- Readings 5.1-5.4

 

- Datapath: System for performing operations on data, plus memory access.
- Control: Control the datapath in response to instructions.


# Simple CPU

Develop complete CPU for subset of instruction set


Memory: lw, sw

Branch: beq


Arithmetic: addi

 

Arithmetic: add, sub

 


Jump: j

 

Most other instructions similar

# Execution Cycle

 

- Obtain instruction from program storage
- Determine required actions and instruction size
- Locate and obtain operand data
- Compute result value or status
- Deposit results in storage for later use
- Determine successor instruction

# Processor Overview

## Overall Dataflow


PC fetches instructions

Instructions select operand registers, ALU immediate values

ALU computes values

Load/Store addresses computed in ALU

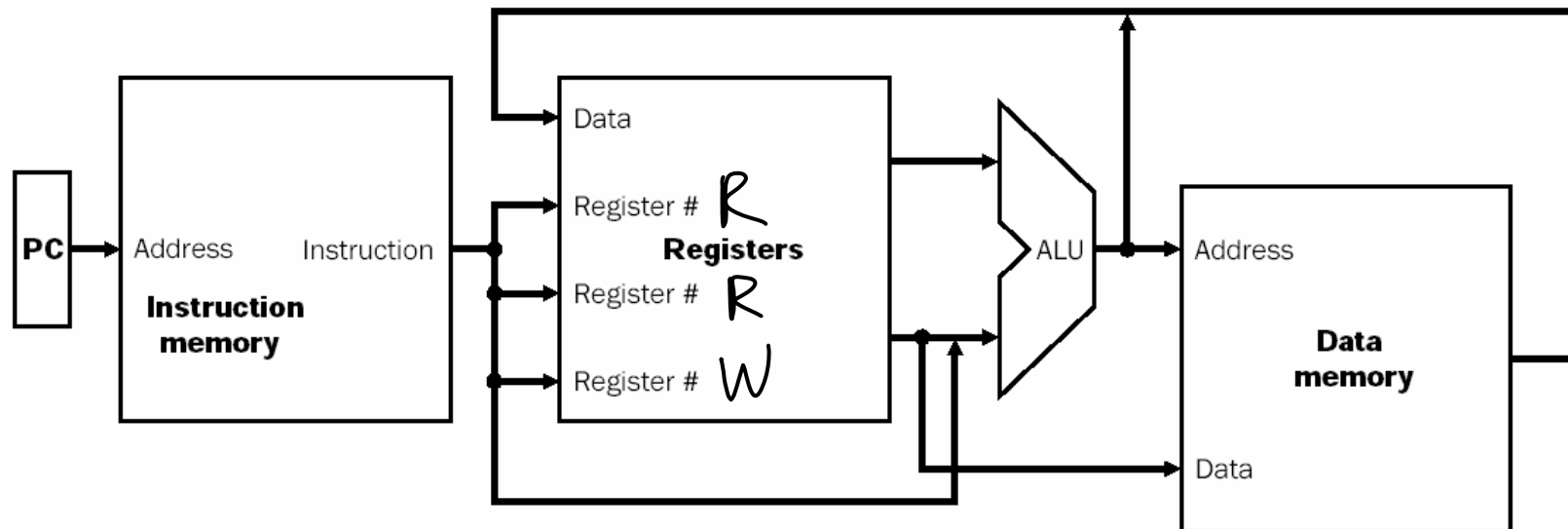Result goes to register file or Data memory



# Processor Design

---

Convert instructions to Register Transfer Level (RTL) specification

Instruction  $\leftarrow$  Memory[PC];


PC  $\leftarrow$  PC + 4;

RTL specifies required interconnection of units

Control designed to achieve given paths for each instruction
 
# Instruction Fetch

```
Instruction = Mem[PC]; // Fetch Instruction  
PC = PC + 4; // Increment PC (32bit)
```



## Add/Subtract RTL

---

Add instruction: `add rd, rs, rt`

`Instruction = Mem[PC];`

`Reg[rd] = Reg[rs] + Reg[rt];`


`PC = PC + 4;`

Subtract instruction: `sub rd, rs, rt`

`Instruction = Mem[PC];`

`Reg[rd] = Reg[rs] - Reg[rt];`


`PC = PC + 4;`

 


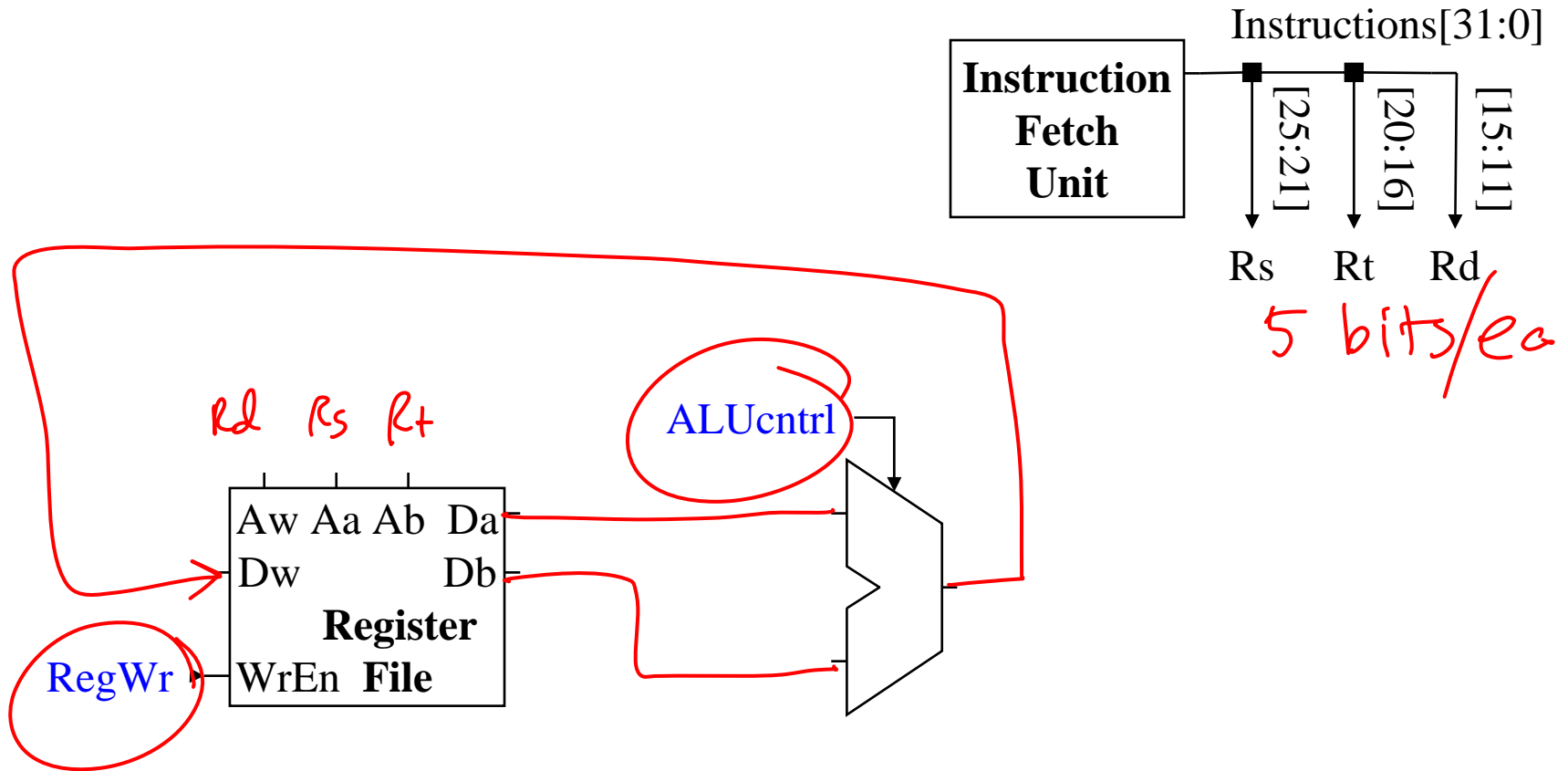
# Datapath for Reg/Reg Ops

$\text{Reg}[\text{rd}] = \text{Reg}[\text{rs}] \text{ op } \text{Reg}[\text{rt}];$



## Add Immediate RTL


Add immediate instruction: `addi rt, rs, imm`

`Instruction = Mem[PC];`

`Reg[rt] = Reg[rs] + SignExtend(imm);`



`PC = PC + 4;`

 31 30 29 28 27 26 25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 09 08 07 06 05 04 03 02 01 00


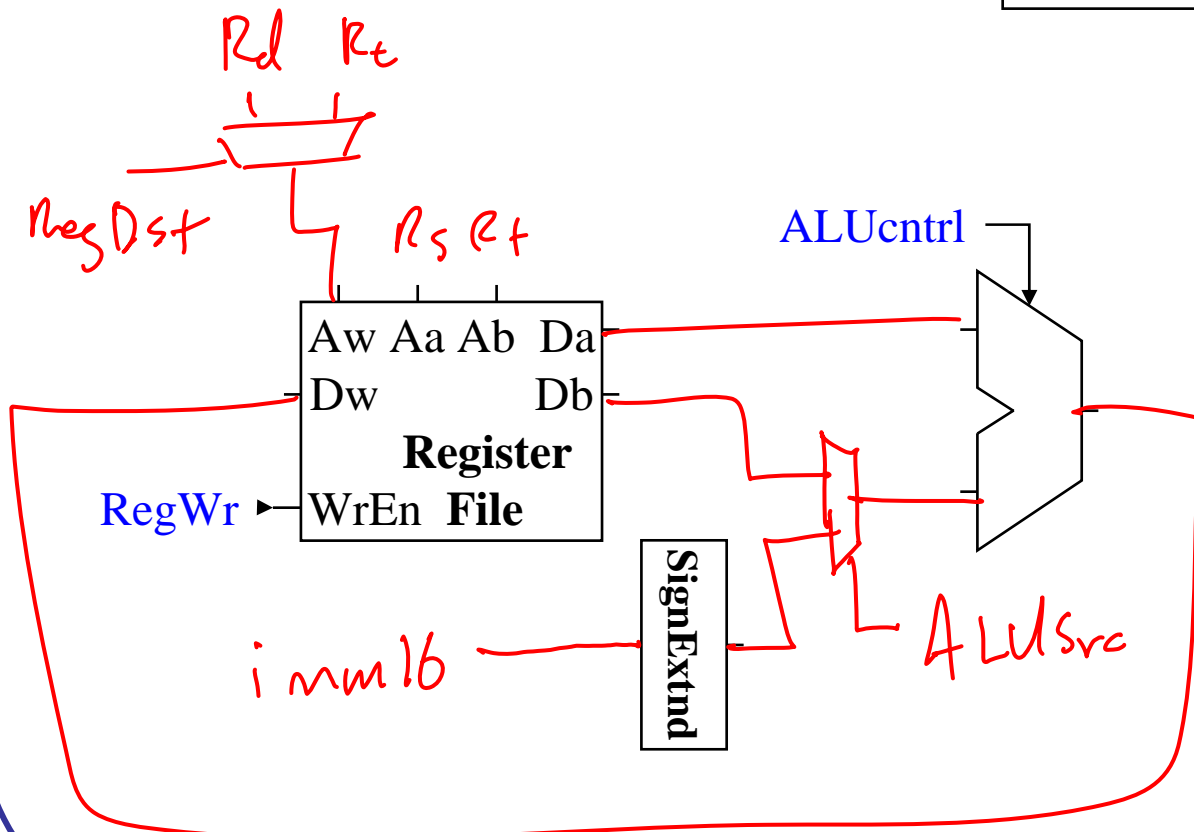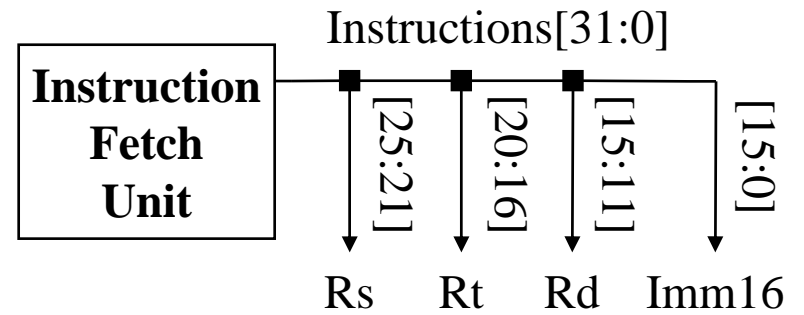
# Datapath + Immediate Ops

$$\text{Reg}[rt] = \text{Reg}[rs] + \text{SignExtend}(\text{imm});$$



## Load RTL


Load Instruction: `lw rt, imm(rs)`

`Instruction = Mem[PC];`

`Addr = Reg[rs] + SignExtend(imm);`


`Reg[rt] = Mem[Addr];`

`PC = PC + 4;`

 
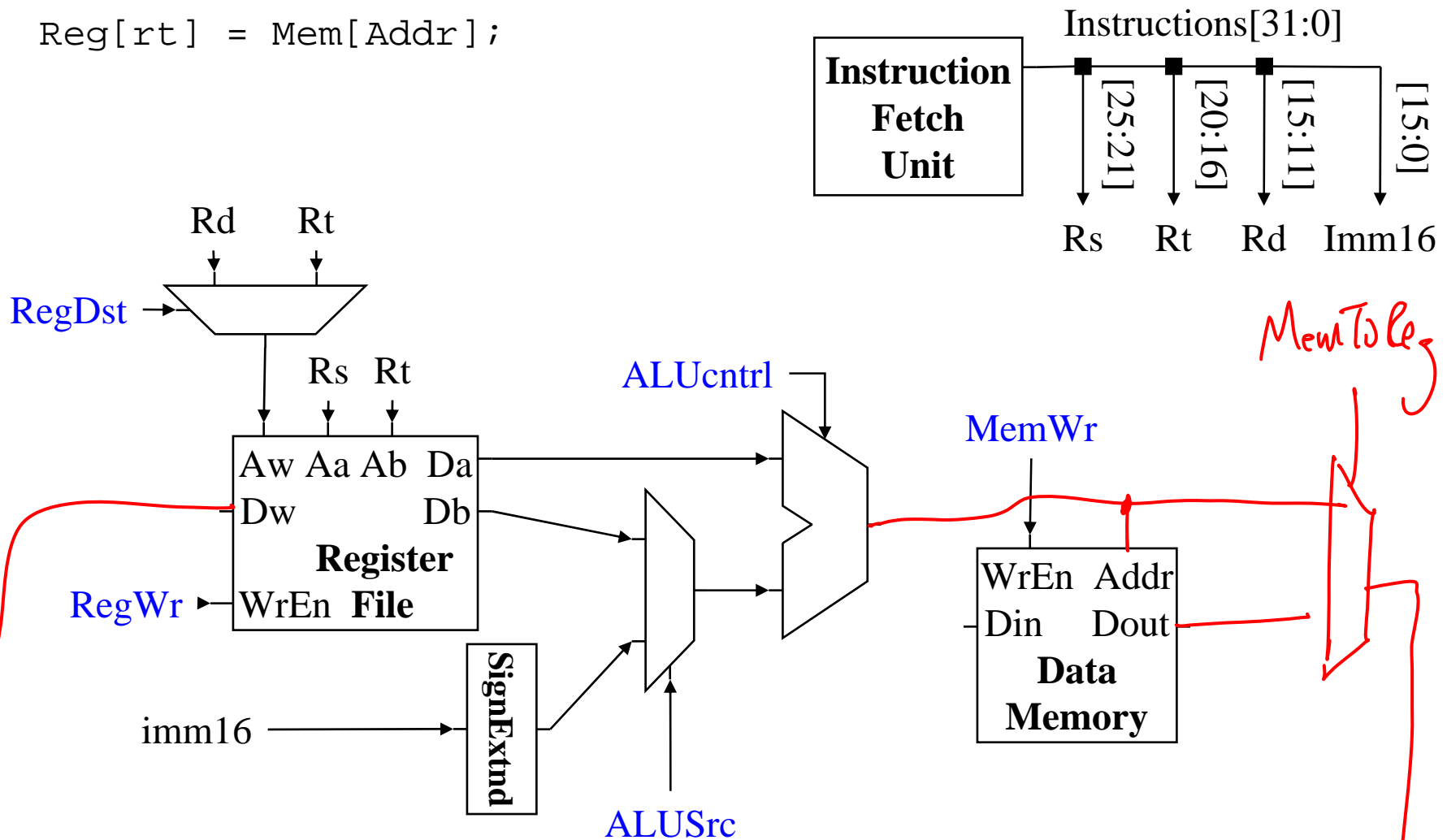
# Datapath + Load

```
Addr = Reg[rs] + SignExtend(imm);  
Reg[rt] = Mem[Addr];
```



## Store RTL


Store Instruction: `sw rt, imm(rs)`

`Instruction = Mem[PC];`

`Addr = Reg[rs] + SignExtend(imm);`

`Mem[Addr] = Reg[rt];`

`PC = PC + 4;`

 


# Datapath + Store

$Addr = Reg[rs] + SignExtend(imm);$

$Mem[Addr] = Reg[rt];$

Note: State of RegWr, MemToReg?

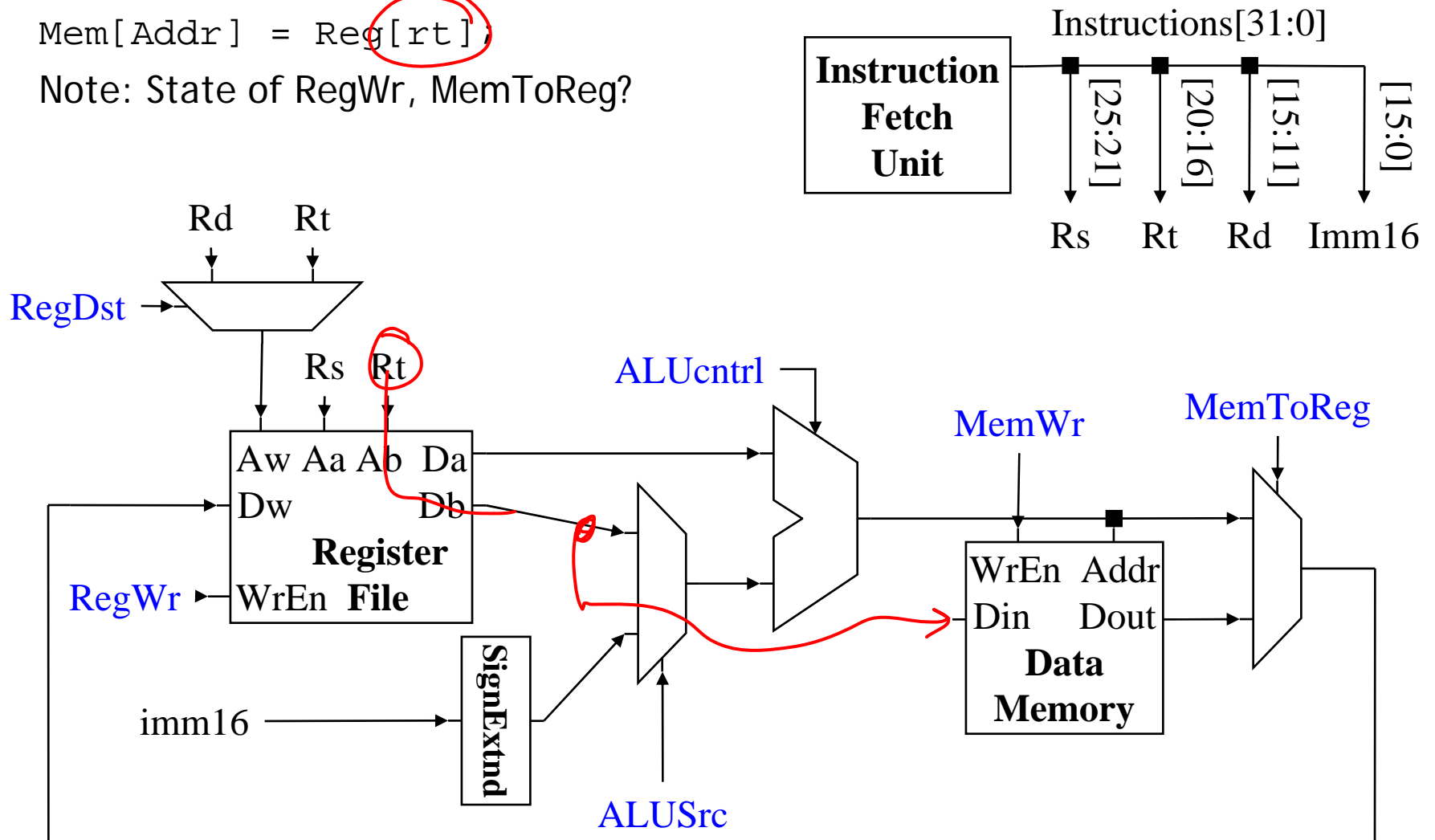

## Branch RTL

Branch Instruction: `beq rs, rt, imm`

```
Instruction = Mem[PC];
```

```
Cond = (Reg[rs] - Reg[rt]) == 0;    // Test equality
```


```
if (Cond)
```

```
    PC = PC + 4 + SignExtend(imm)*4;    // Neg for backward  
                                         // *4: LSbits == 00
```

```
else
```

```
    PC = PC + 4;
```

 31 30 29 28 27 26 25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 09 08 07 06 05 04 03 02 01 00





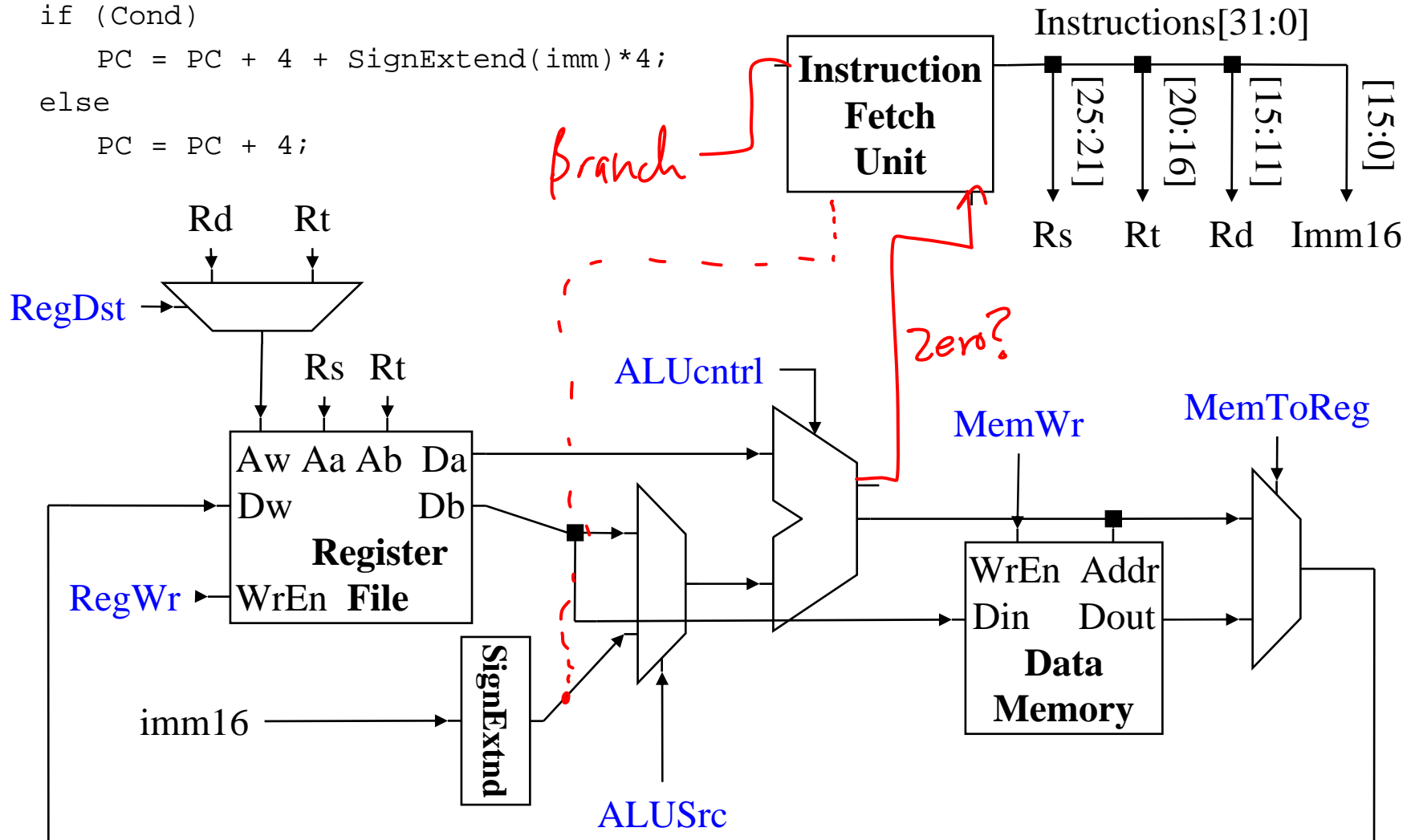
# Datapath + Branch


```

Cond = (Reg[rs] - Reg[rt]) == 0;
if (Cond)
    PC = PC + 4 + SignExtend(imm)*4;
else
    PC = PC + 4;
    
```


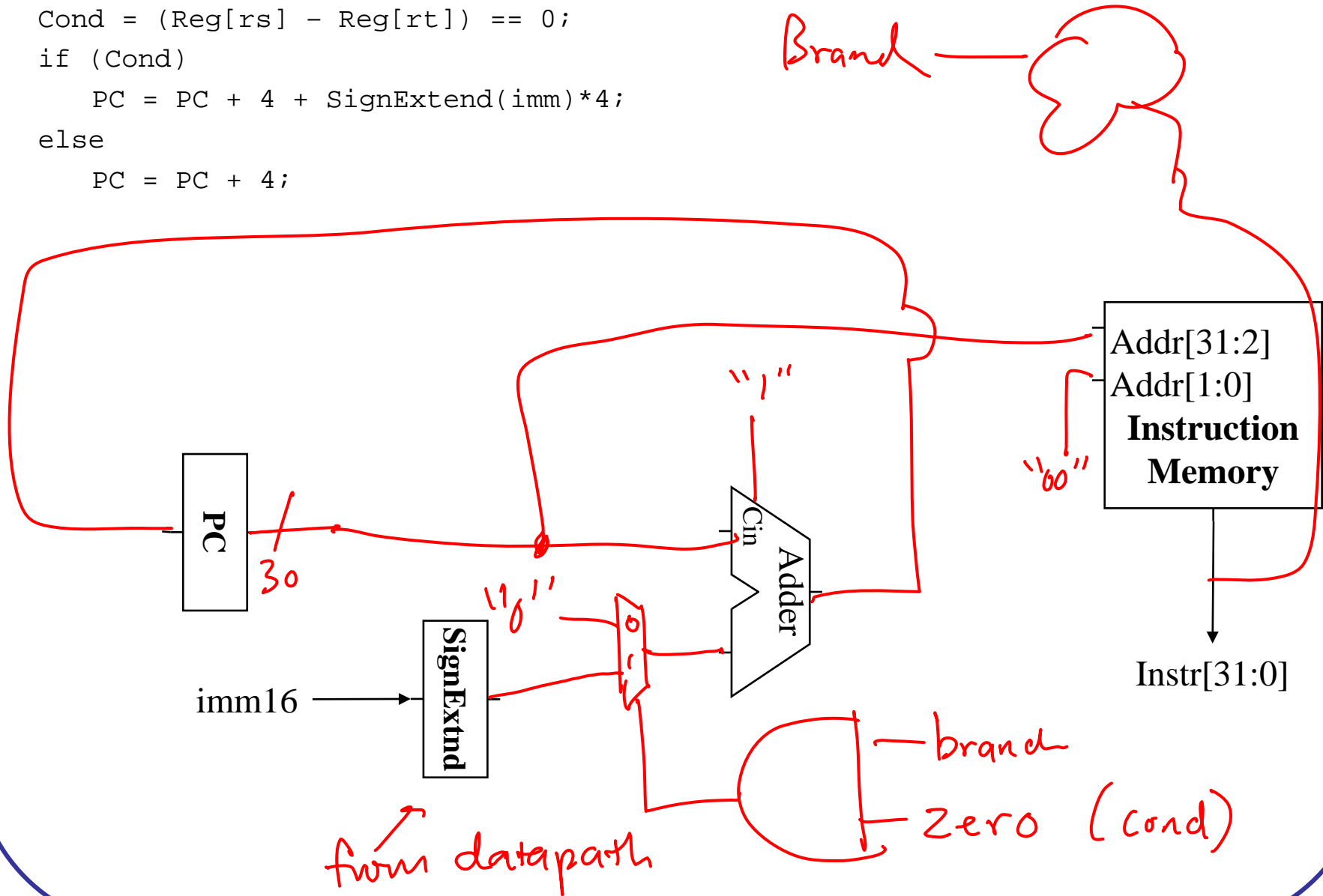
# Instruction Fetch + Branch

```
Cond = (Reg[rs] - Reg[rt]) == 0;  
if (Cond)  
    PC = PC + 4 + SignExtend(imm)*4;  
else  
    PC = PC + 4;
```




## Jump RTL

---

Store Instruction: j target


```
Instruction = Mem[PC];
```
 
```
PC = { PC[31:28], target[25:0], "00" };
```



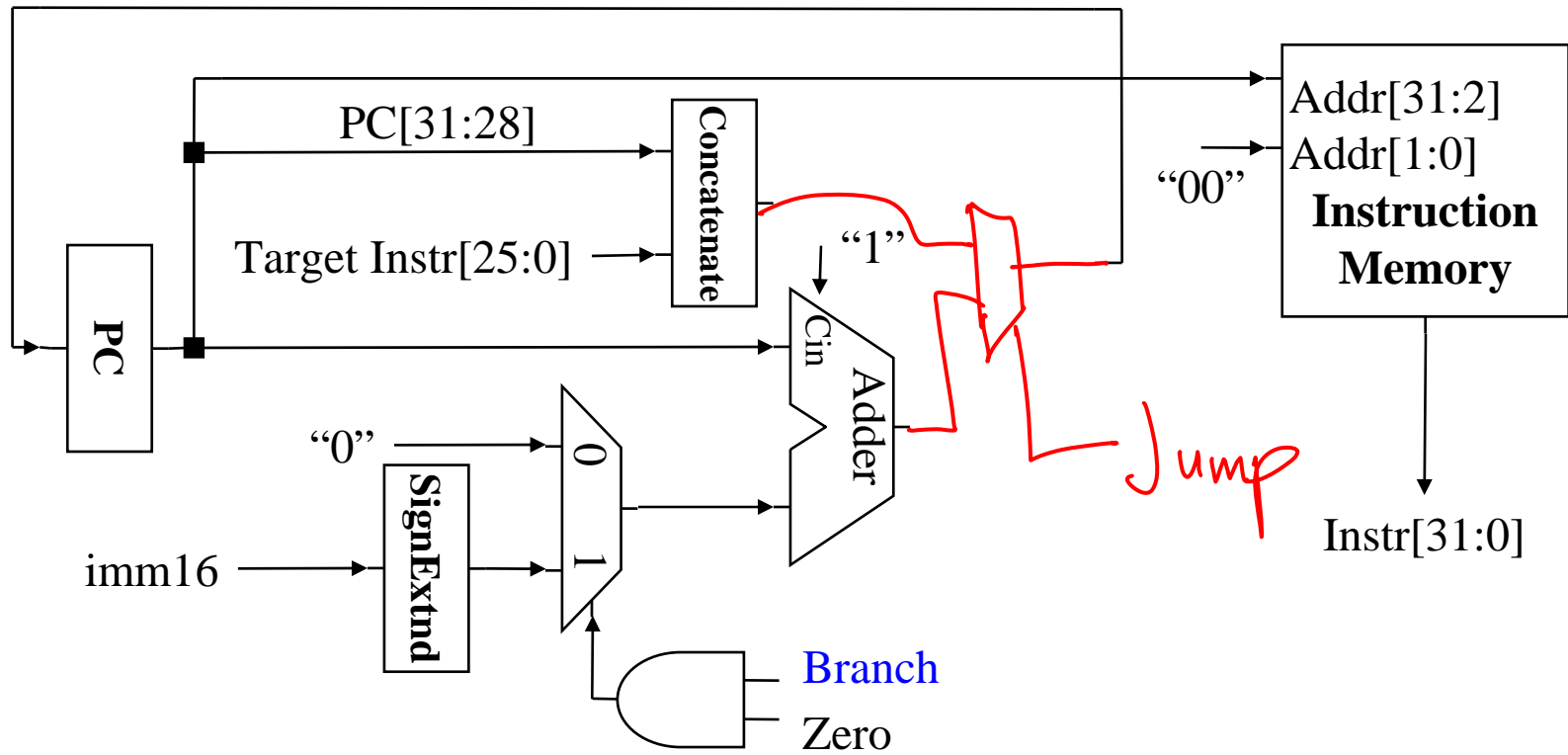
# Instruction Fetch + Jump


$PC = \{ PC[31:28], target[25:0], "00" \};$



# Complete Datapath

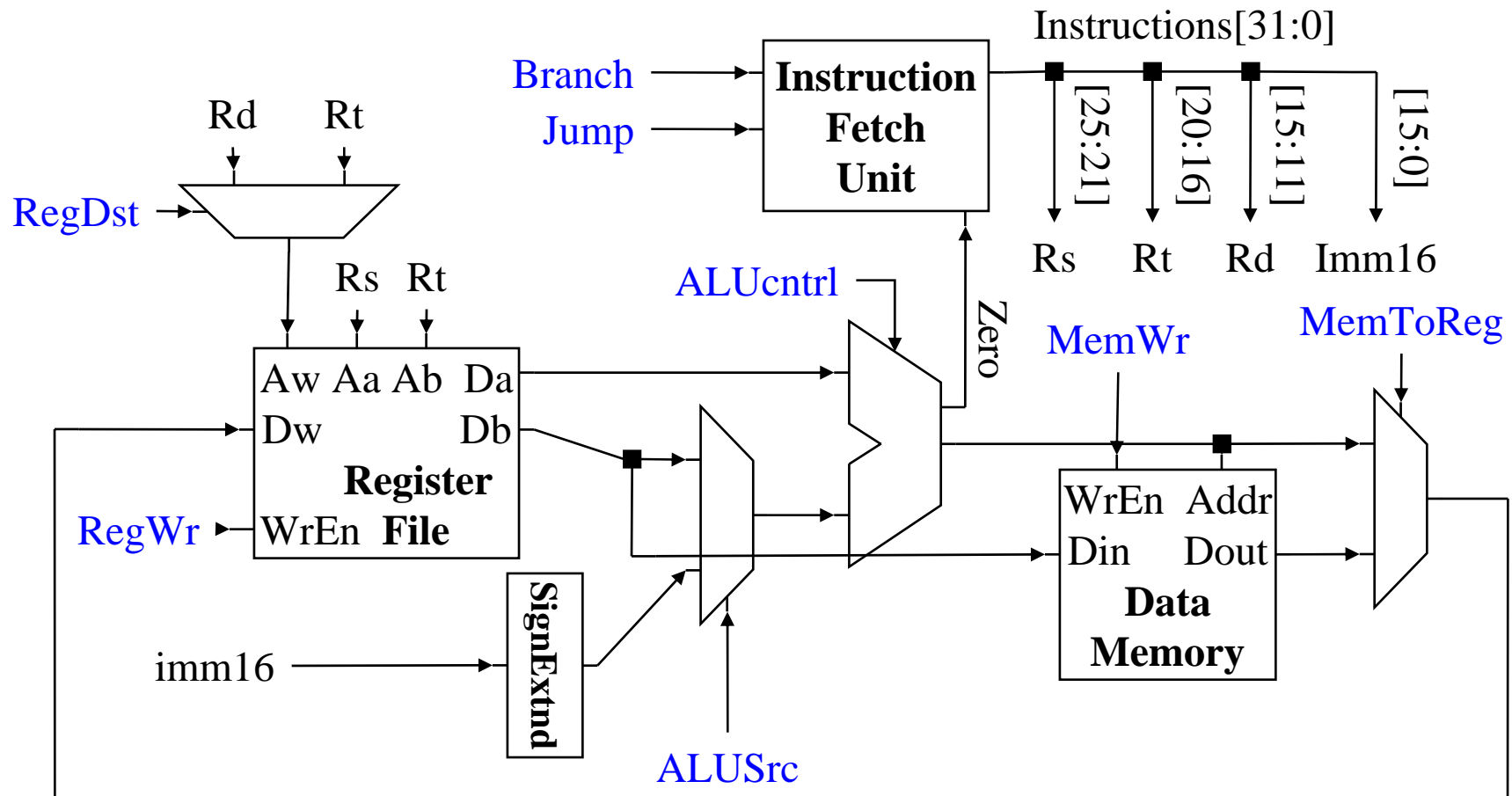

# Complete Fetch Unit

 

# Control

---

- Identify control points for pieces of datapath
  - Instruction Fetch Unit
  - ALU
  - Memories
  - Datapath muxes
  - Etc.
- Use RTL for determine per-instruction control assignments

# Control Signals



Func	10000 <sup>0</sup>	100010	XXX	XXX	XXX	XXX
Op	000000	000000	100011	101011	000100	000010
	add	sub	lw	sw	beq	j
<i>Reg Dst</i>						
<i>ALU Src</i>						
<i>Mem To Reg</i>						


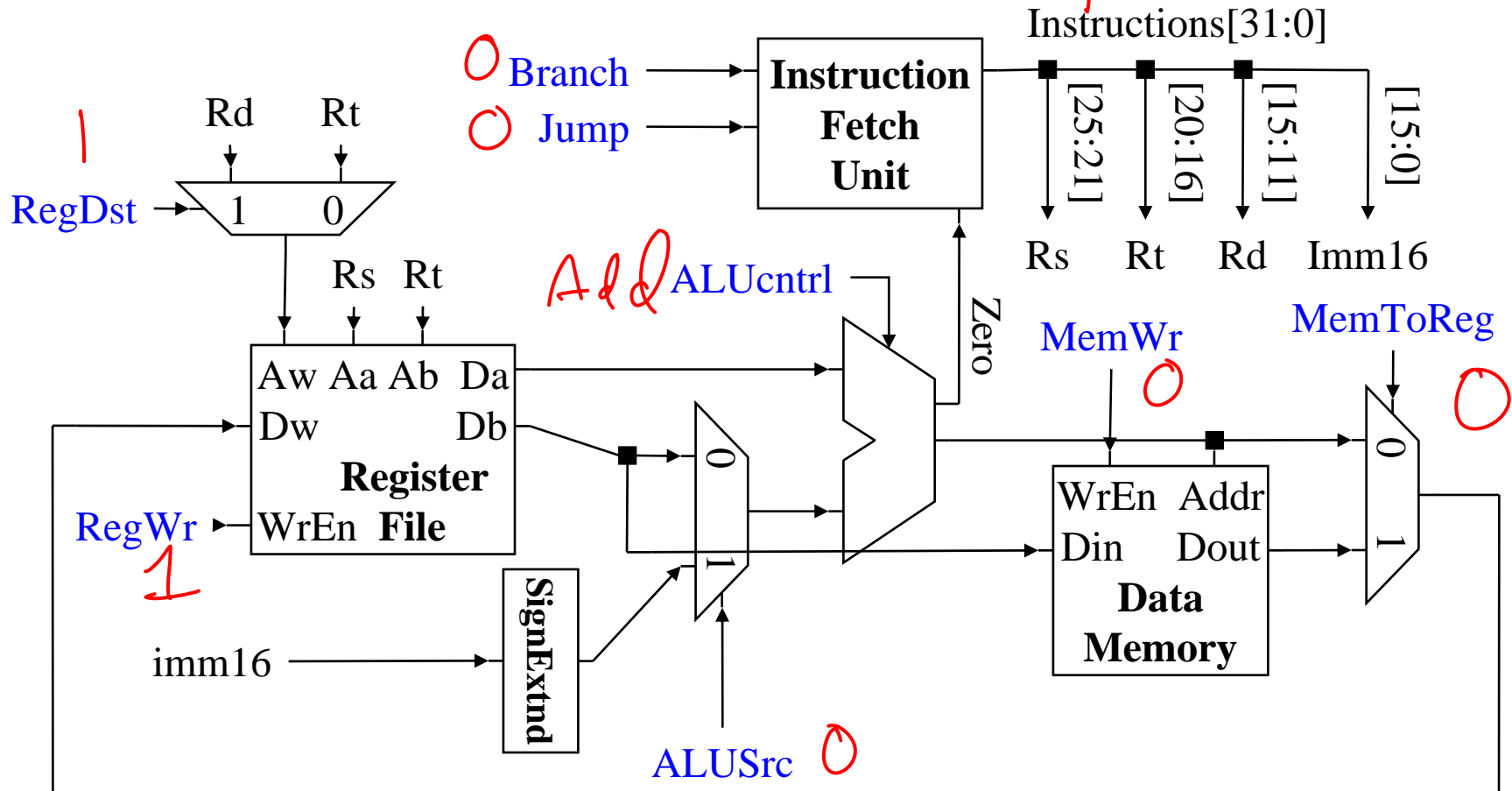 
# Add Control

```


add rd, rs, rt
Instruction = Mem[PC];
Reg[rd] = Reg[rs] + Reg[rt];
PC = PC + 4;
    
```


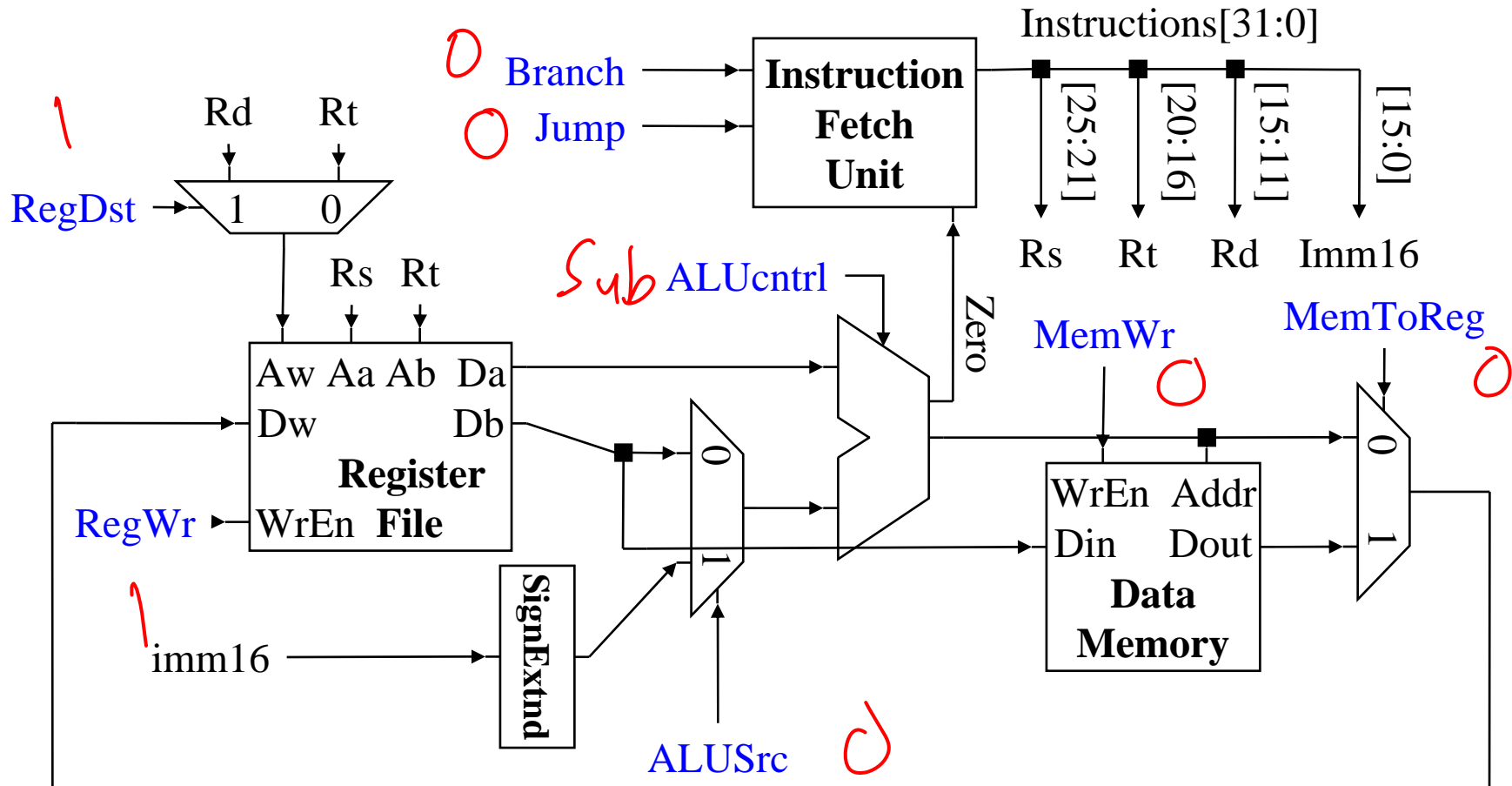
# Subtract Control

```

sub rd, rs, rt
Instruction = Mem[PC];
Reg[rd] = Reg[rs] - Reg[rt];
PC = PC + 4;
    
```



# Load Control


```
lw rt, imm(rs)
```

```
Instruction = Mem[PC];
```

```
Addr = Reg[rs] + SignExtend(imm);
```


```
Reg[rt] = Mem[Addr];
```

```
PC = PC + 4;
```

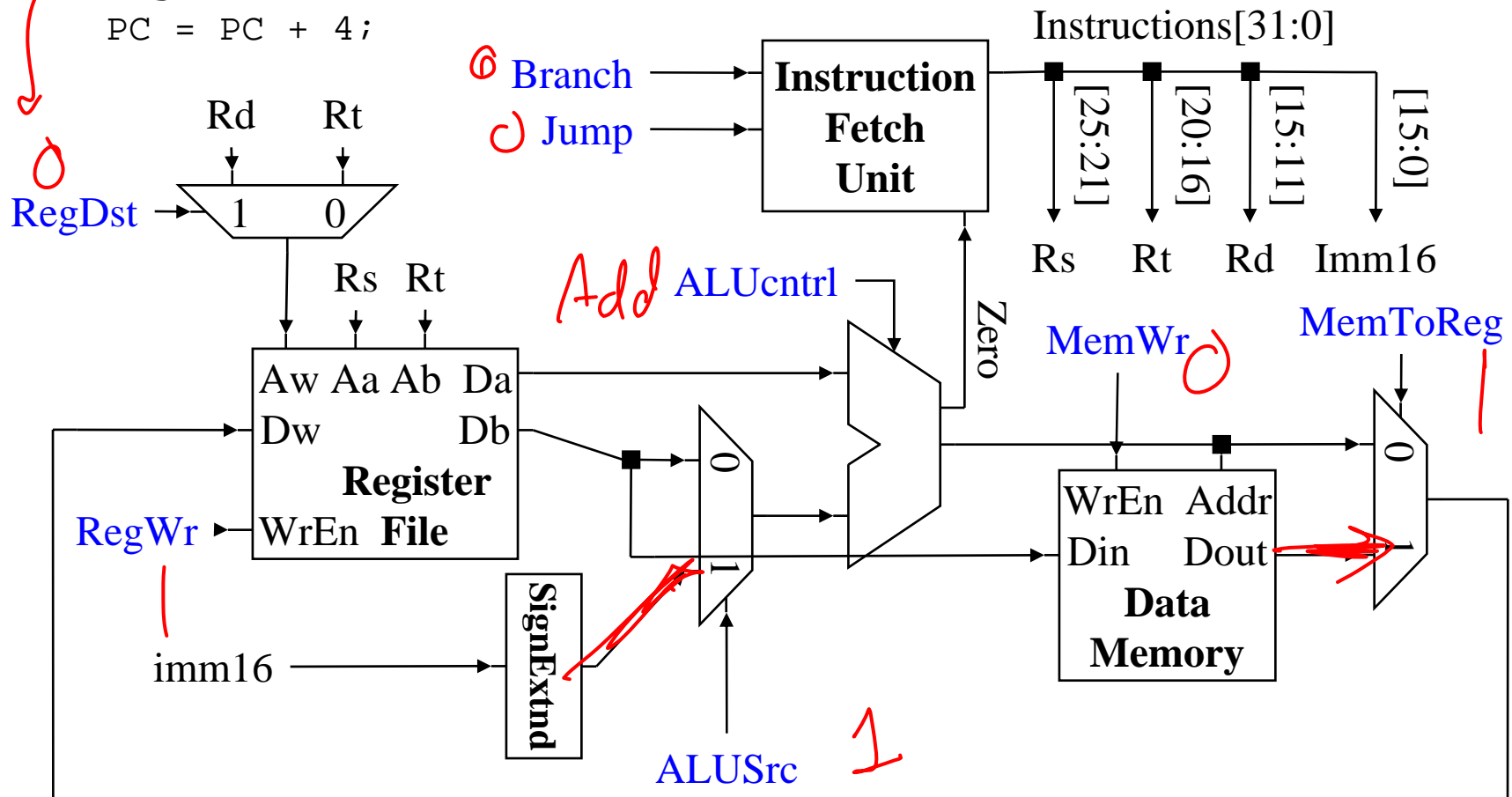
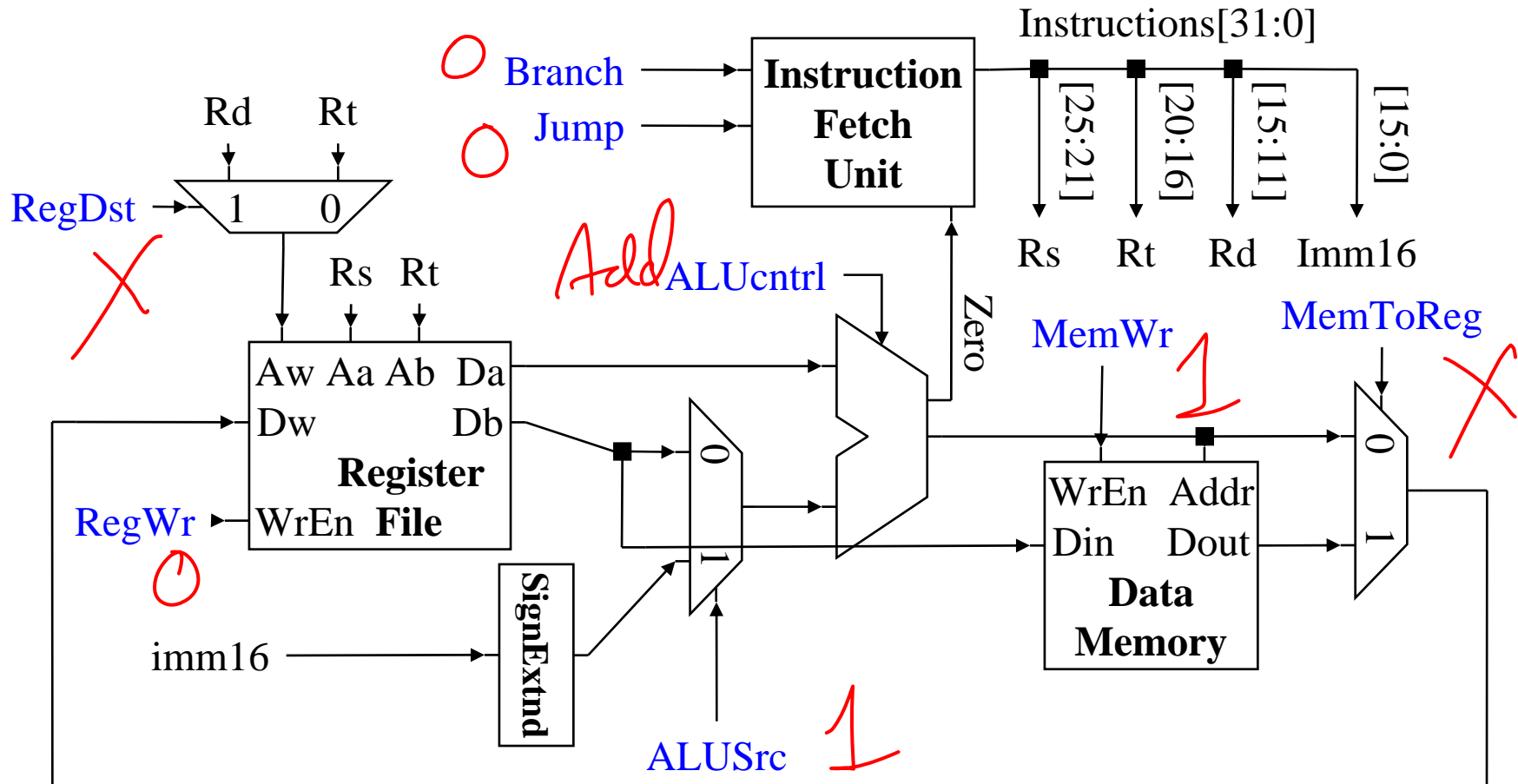
# Store Control

```
sw rt, imm(rs)
Instruction = Mem[PC];
Addr = Reg[rs] + SignExtend(imm);
Mem[Addr] = Reg[rt];
```



# Branch Control


```
beq rs, rt, imm
```

```
Instruction = Mem[PC];
```

```
Cond = (Reg[rs] - Reg[rt]) == 0;
```


```
if (Cond) PC = PC+4+SignExtend(imm)*4;
```

```
else PC = PC + 4;
```

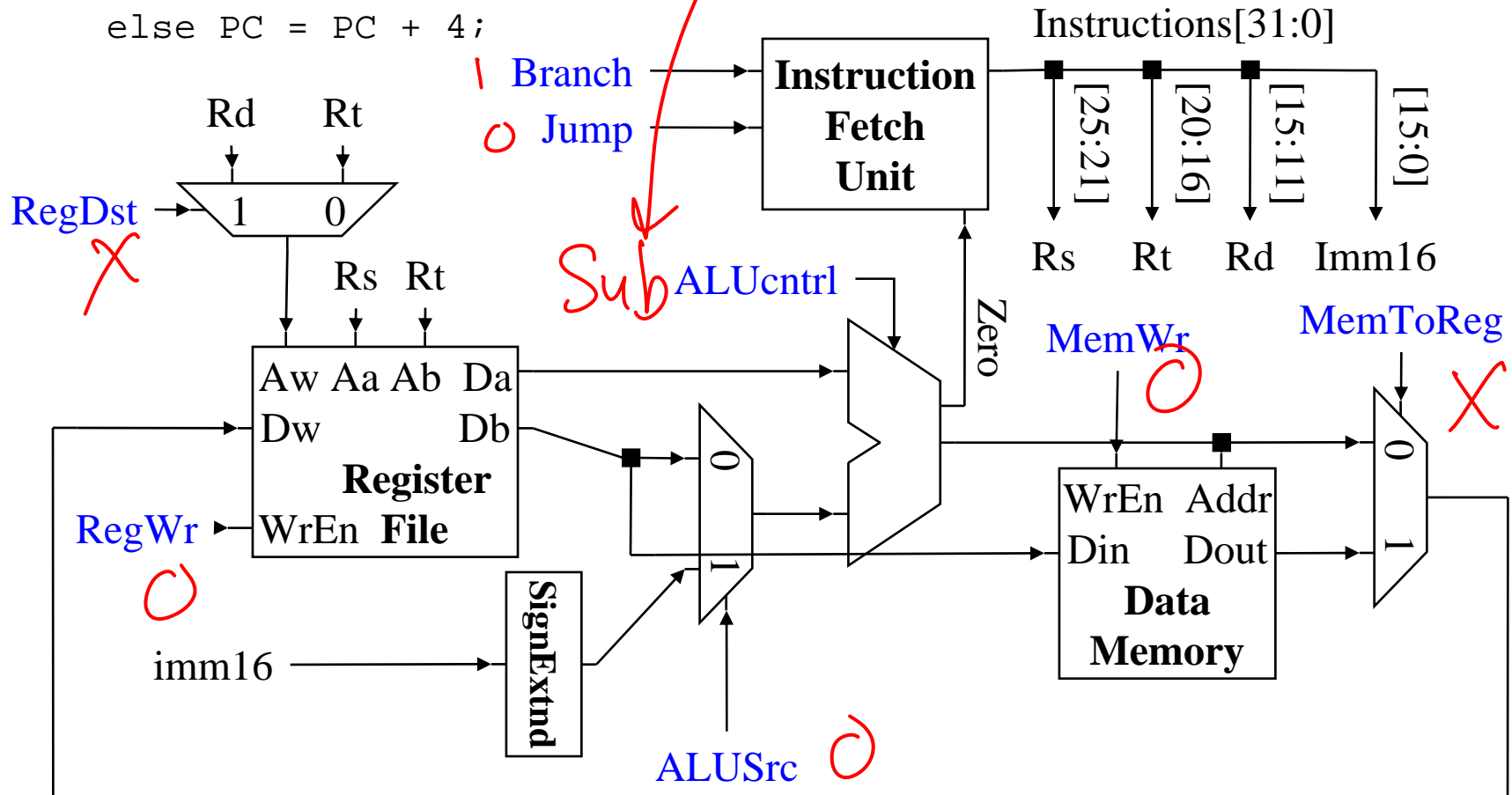
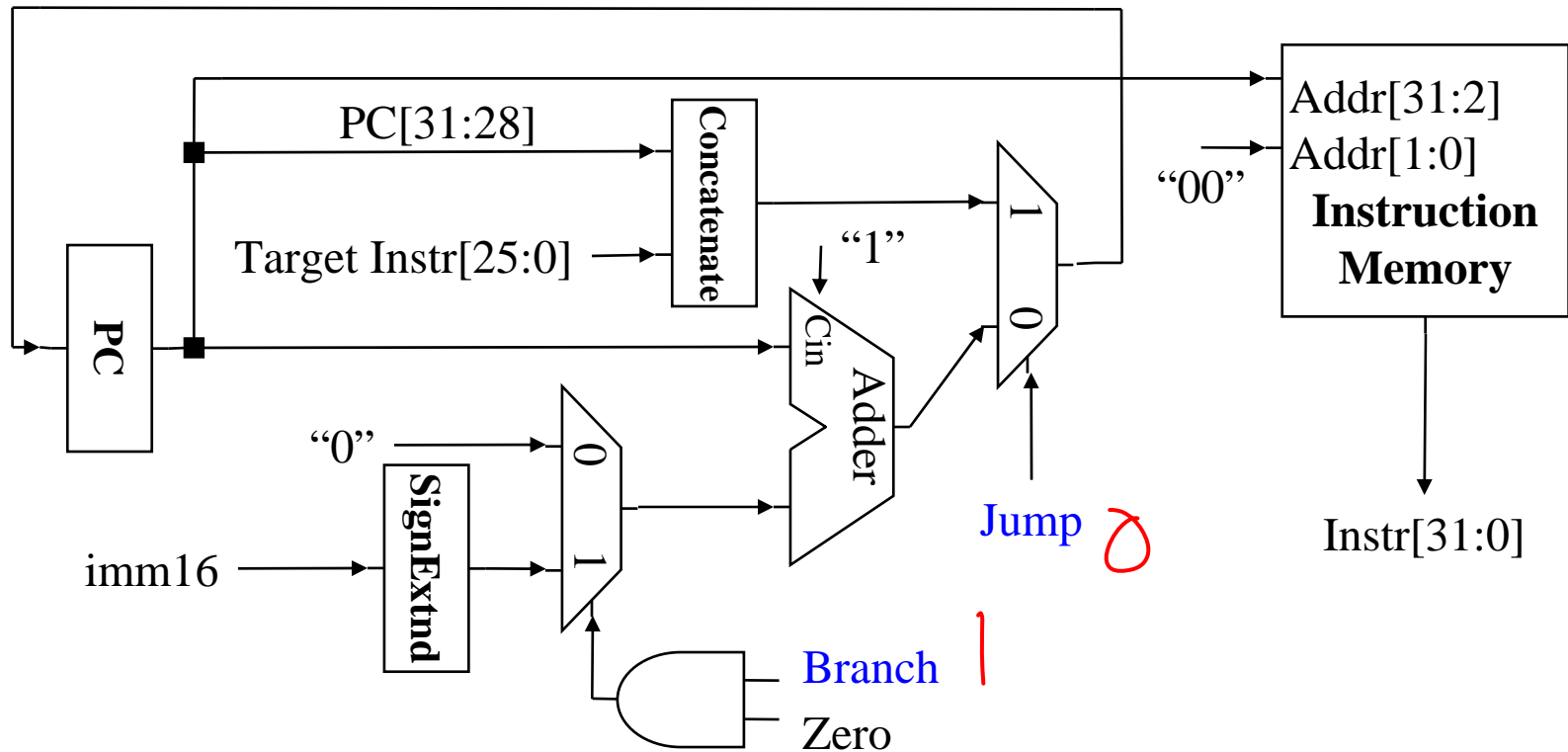
## Branch Control (cont.)


```
beq rs, rt, imm
Instruction = Mem[PC];
Cond = (Reg[rs] - Reg[rt]) == 0;
if (Cond) PC = PC+4+SignExtend(imm)*4;
else PC = PC + 4;
```


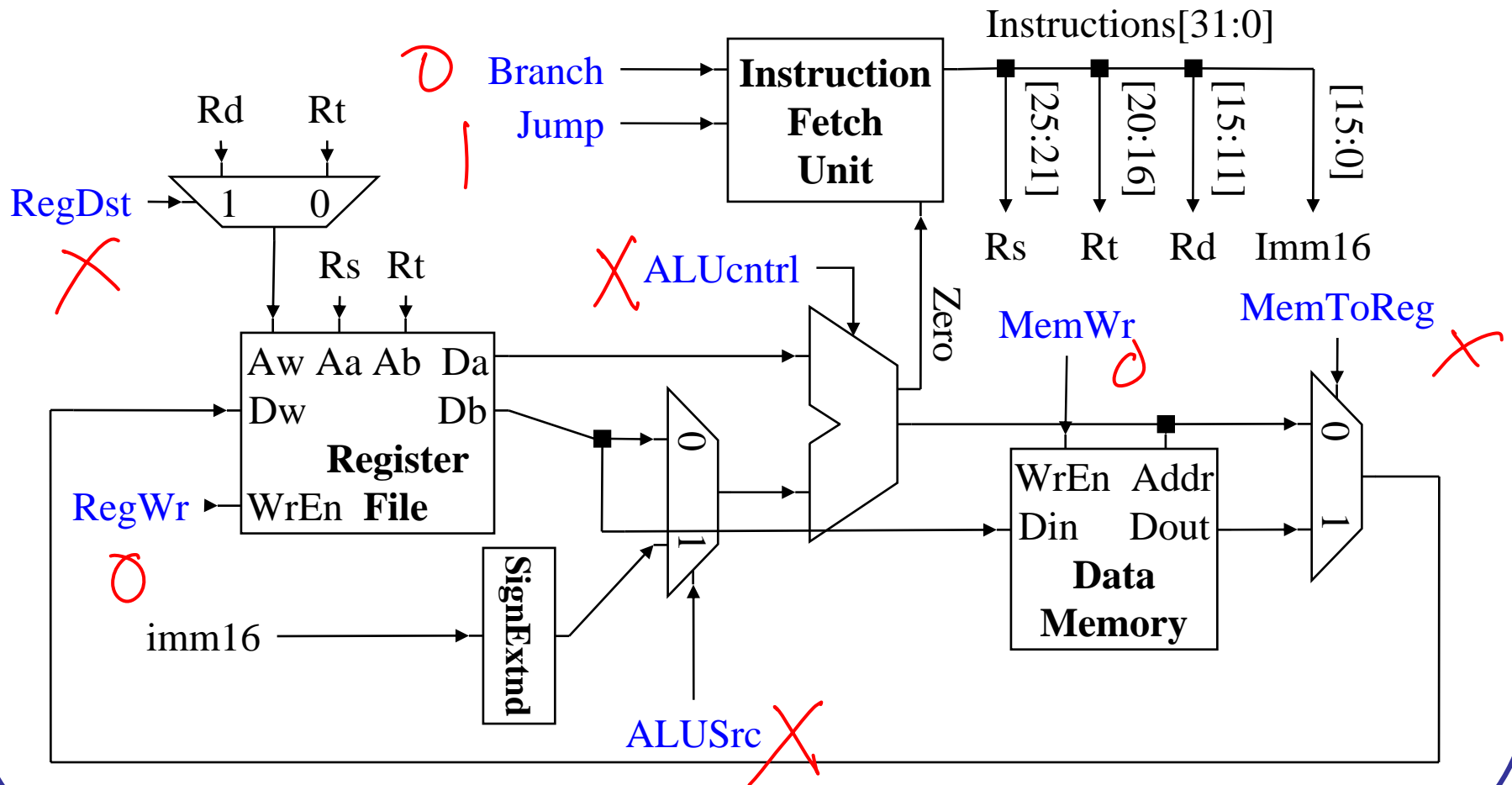
# Jump Control

```

j target
Instruction = Mem[PC];
PC = { PC[31:28], target[25:0], "00" };
    
```




## Jump Control (cont.)

j target

```
Instruction = Mem[PC];
```
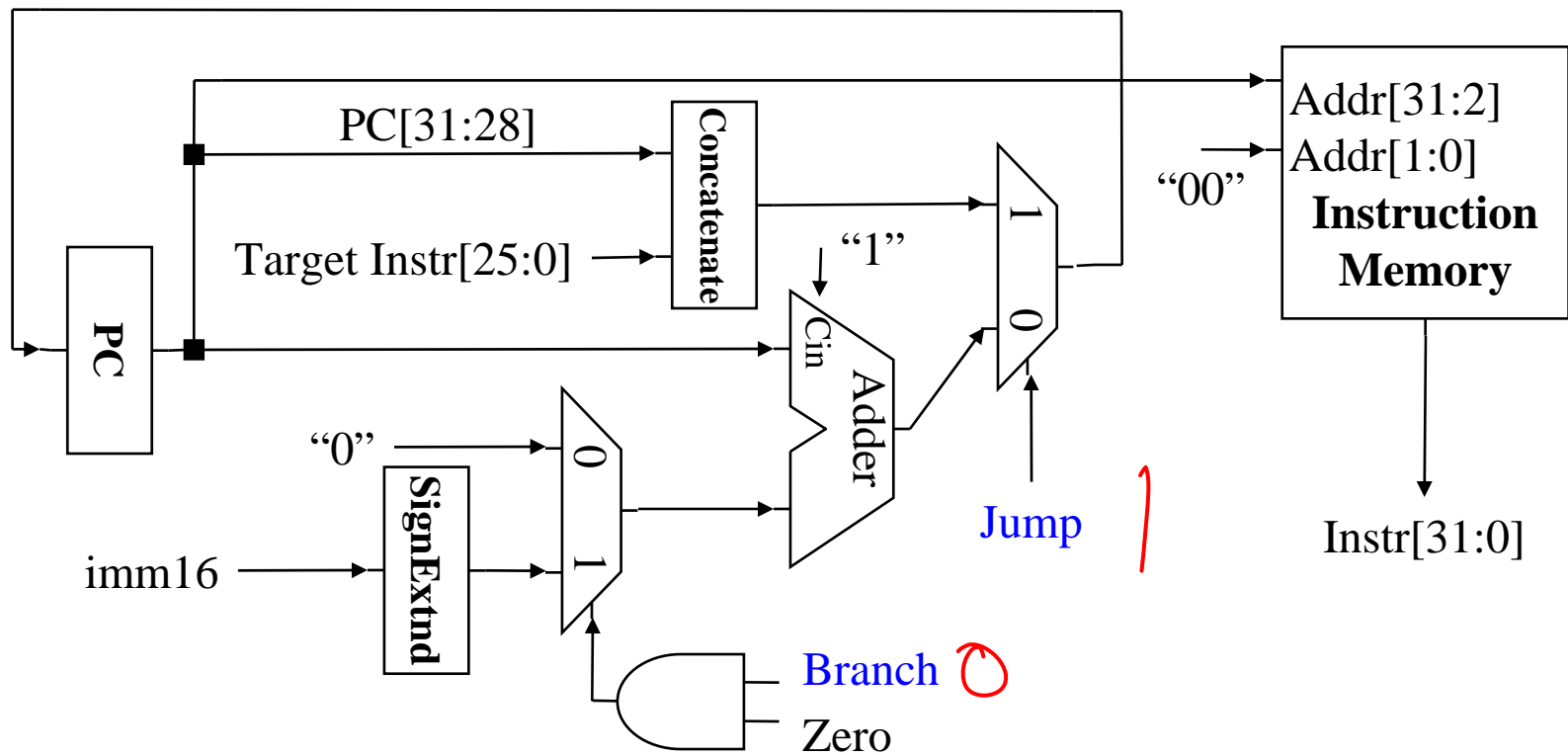
```
PC = { PC[31:28], target[25:0], "00" };
```





## Control Signals

Func	10000	100010	XXX	XXX	XXX	XXX
Op	000000	000000	100011	101011	000100	000010
	add	sub	lw	sw	beq	j
RegDst	1	1	0	X	X	X
ALUSrc	0	0	1	1	0	X
MemToReg	0	0	1	X	X	X
RegWr	1	1	1	0	0	0
MemWr	0	0	0	1	0	0
Branch	0	0	0	0	1	X
Jump	0	0	0	0	0	1
ALUCntrl	Add	Sub	Add	Add	Sub	X