

110

Arithmetic

ENGR 3410 - Computer Architecture

Mark L. Chang

Fall 2007

Computer Arithmetic


- Readings: Chapter 3
- Review binary numbers, 2's complement
- Develop Arithmetic Logic Units (ALUs) to perform CPU functions.
- Introduce multiplication, division, floating point.

Full Adder

A	B	CI	CO	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
→ 0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$CO = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

$$= BC + AC + AB$$

 


$$S = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

$$= A \oplus B \oplus C$$

 

Multi-Bit Addition

Cascaded Multi-bit Adder


 


usually interested in adding more than two bits

this motivates the need for the full adder

Adder/Subtractor

Mux

  

Instruction Register


LOGIC

SUB

$$A - B = A + (-B) = A + \overline{B} + 1$$


ALU: Arithmetic Logic Unit

 - Computes arithmetic & logic functions based on controls
 - Add, subtract
 - XOR, AND, NAND, OR, NOR
 - ==, <, overflow, ...




Bit Slice ALU Design

- Add, Subtract, AND, OR

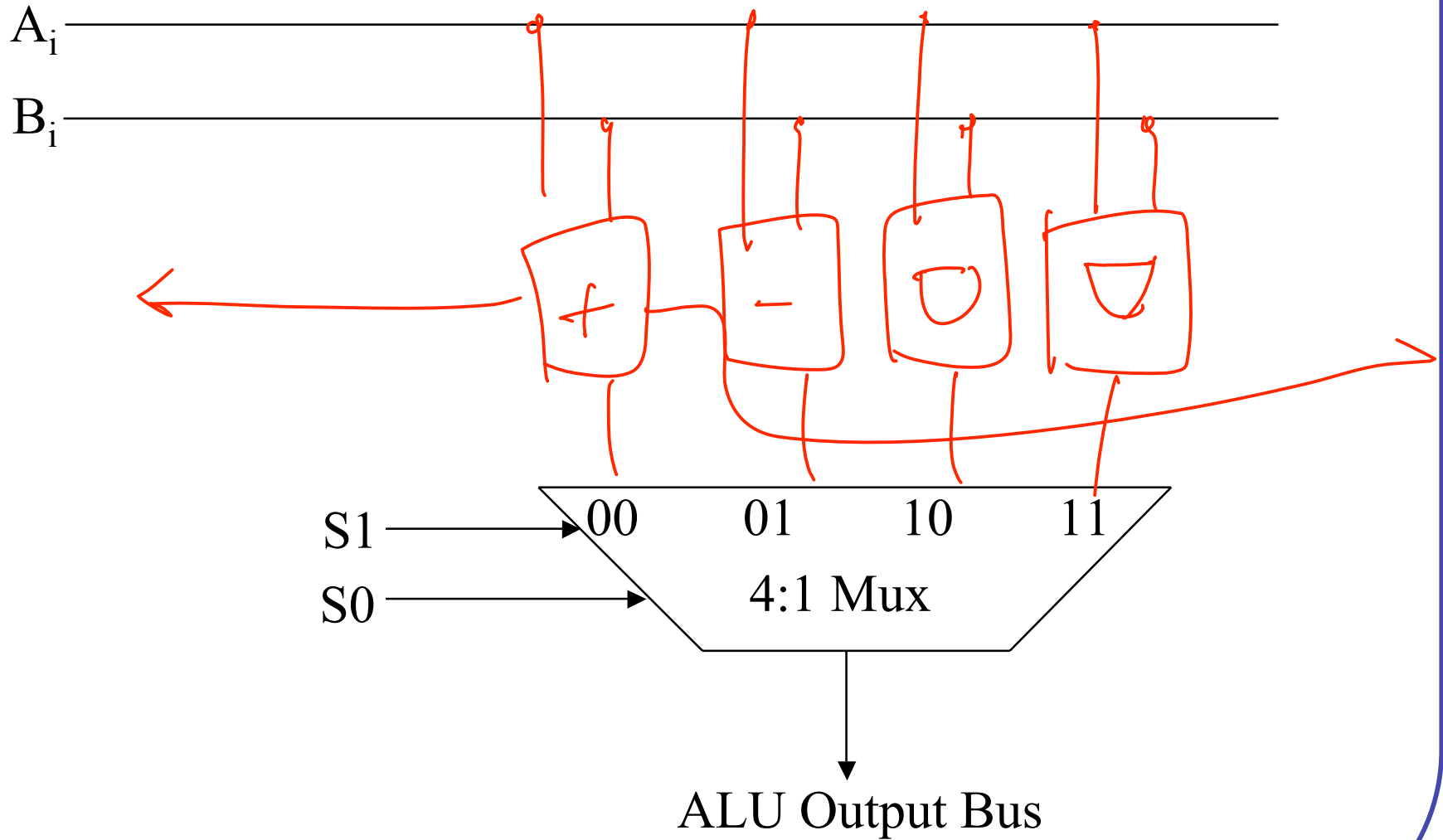


Bit Slice ALU Design (cont.)

 - Route Carries
- Overflow, zero, negative



SLT

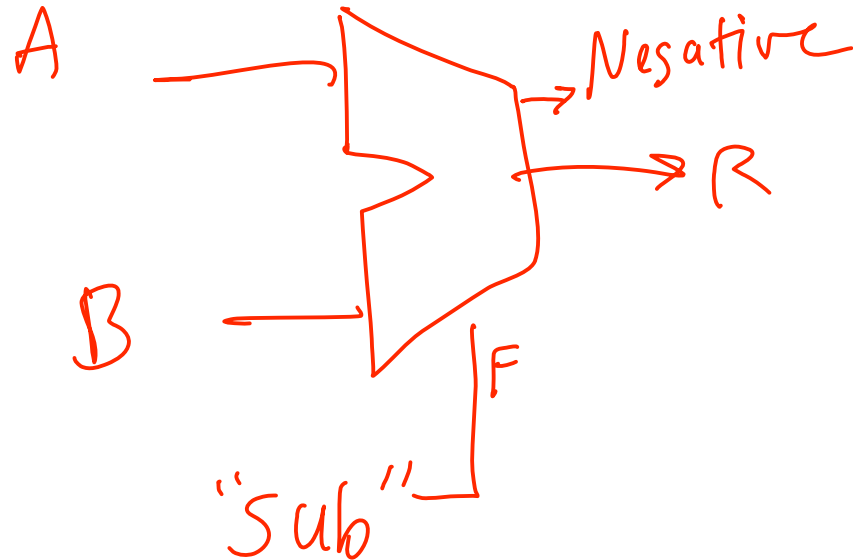- Set less than: if $(A < B)$ then $R = 1$, else $R = 0$
 - How do we know if $(A < B)$
 - Interaction w/overflow




Shifter

07


- Support shift operations: $(A \ll 01101)$

- Optional shift by one: $(A \ll b_0)$

 

- Optional shift by two: $(A \ll b_1)$

Shifter (cont.)

 

Multiplication

- Example

Multiplicand: 0 1 1 0 6
Multiplier: 0 1 0 1 5

→ 0 1 1 0
 0 0 0 0
 0 1 1 0
 0 0 0 0

4 partial products

30


Repeat n times:

Compute partial product; shift; add



NOTE: Each bit of partial products is just an AND operation

Sequential Multipliers

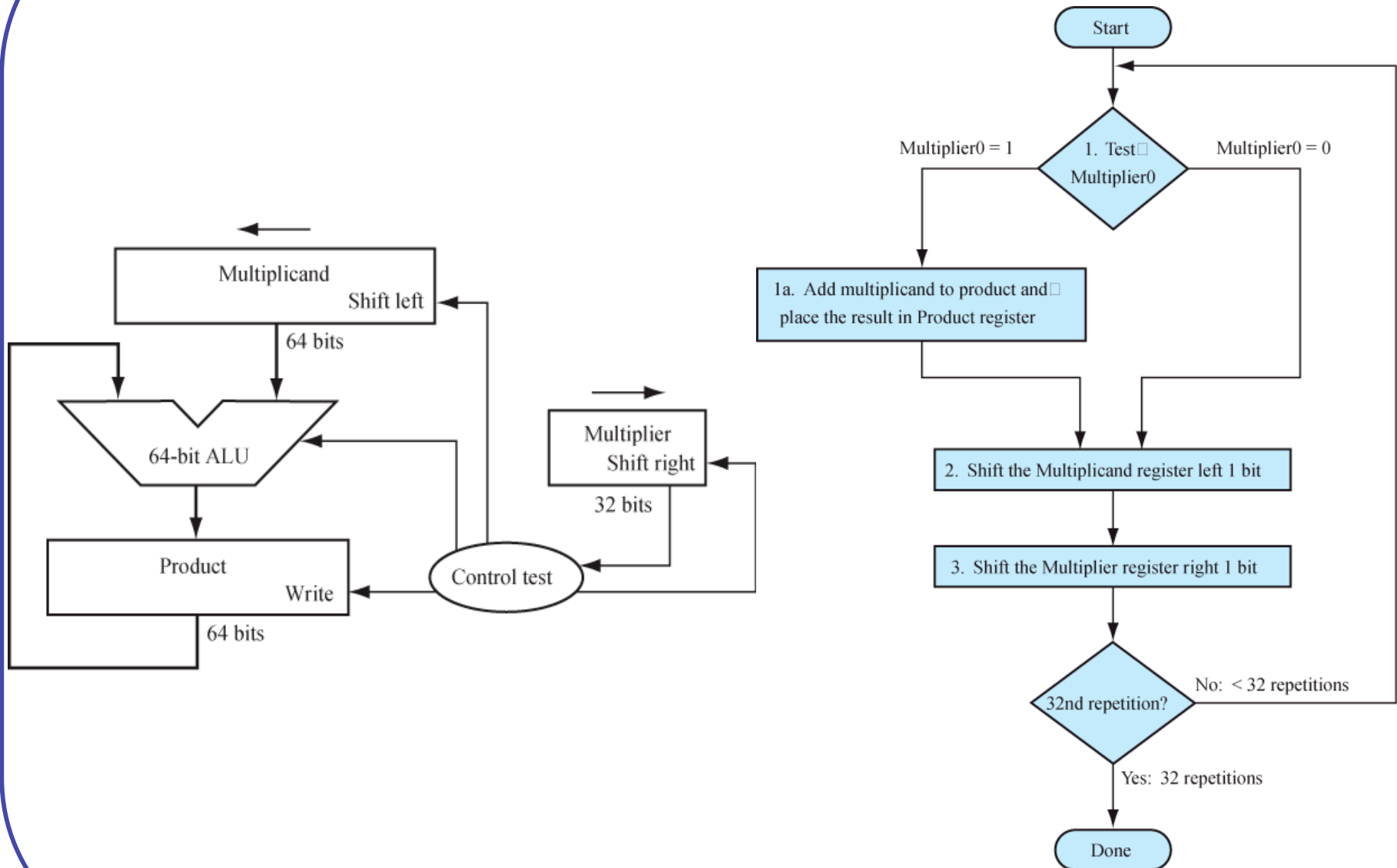


Division

- Example

Divisor: 0010 (2) $\overline{0 \ 1 \ 1 \ 0}$ **(6) Dividend**

Sequential Dividers

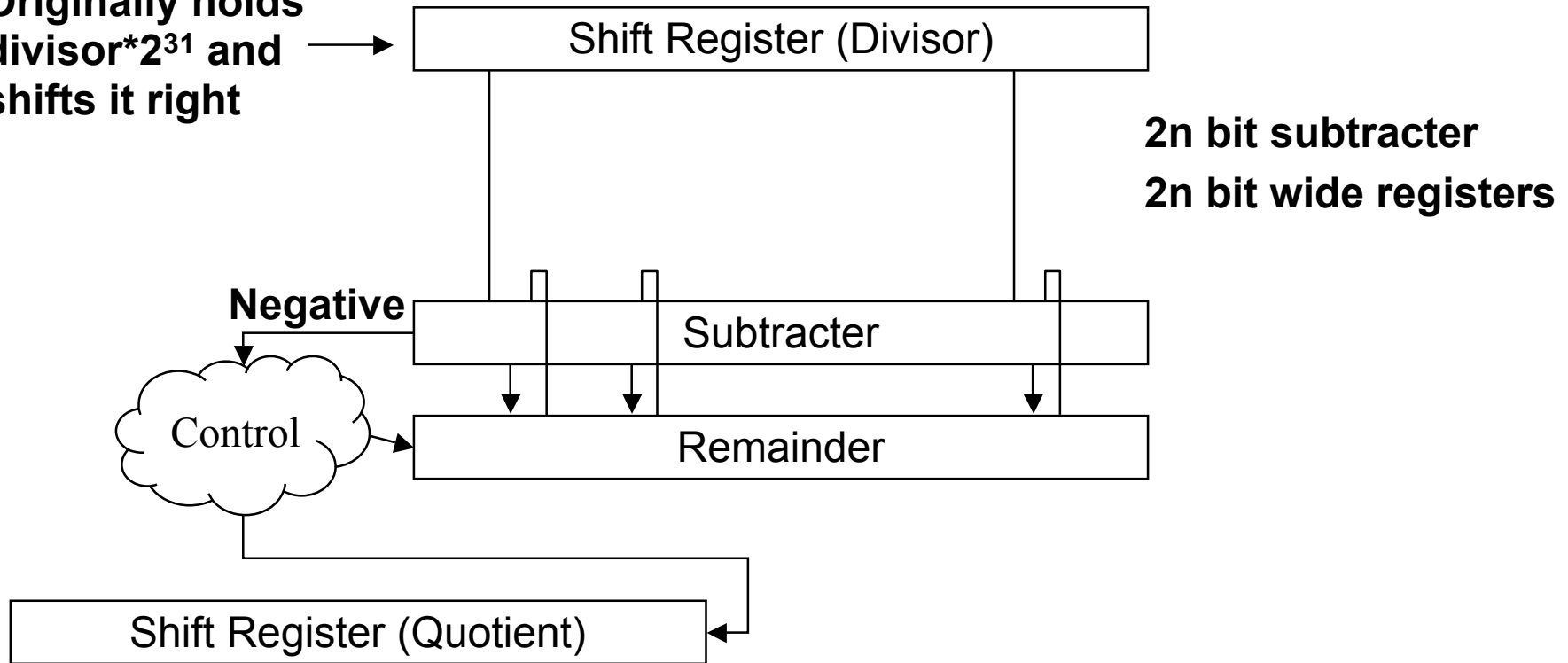Originally holds
divisor* 2^{31} and
shifts it right



Remainder

Alternatively:

Shift remainder register to left
Use only n-bit subtracter

Floating Point

Want to represent numbers outside $2^{31}-1 \dots -2^{31}$

Ideal: ~Scientific Notation

$$(+/-)\text{Significand} * \text{Base}^{\text{Exponent}} \quad 5.439 * 10^{12} \quad 1.010010 * 2^{100101}$$

Multiplication:

$$(5.1 * 10^{12}) * (-2.0 * 10^{-3})$$

Sign:

$(-)$

Exponent:

Add exponents = 9

Significand:

$$S_1 * S_2 = 10.2$$

$$\rightarrow [-1.02 * 10^{10}]$$

Floating Point Addition

Addition: $(5.38 * 10^5) + (4.99 * 10^5)$

$(9.99 * 10^4) + (-1.0 * 10^5)$

$5.38 \times 10^5 + 4.99 \times 10^5$

$0.999 \times 10^5 + -1.0 \times 10^5$

Sign: Bigger value

Exponent: (+) Bigger value

Significand: Do ⁵ add/sub


10.37
 1.037×10^6

(-)
 5

0.001
 1.0×10^2

Floating Point Representation

- Floating Point (Float) = $(-1)^s * (1.\text{significantand}) * 2^{(\text{exponent}-127)}$

 

IEEE.754

- 0.75 in Floating Point?

sign: 1

sig: 1. sig. (1.100000)


exp: $-1 = \text{exp} - 127$
 $\text{exp} = 126$

1.0

0.1 = $1/2$

0.01 = $1/4$

 0.11 = 0.75 $\rightarrow 1.1 \times 2^{-1}$




126_{10}

0

Double Precision Representation

 - Double Precision (double) = $(-1)^s * (1.\text{significand}) * 2^{(\text{exponent}-1023)}$



- -0.75 in Double Precision?

