

111

Single Cycle CPU


ENGR 3410 - Computer Architecture

Mark L. Chang

Fall 2007

Datapath & Control

- Readings 5.1-5.4

 

- Datapath: System for performing operations on data, plus memory access.
- Control: Control the datapath in response to instructions.


Simple CPU

Develop complete CPU for subset of instruction set


Memory: lw, sw

Branch: beq


Arithmetic: addi

 

Arithmetic: add, sub

 


Jump: j

 

Most other instructions similar

Execution Cycle

 

- Obtain instruction from program storage
- Determine required actions and instruction size
- Locate and obtain operand data
- Compute result value or status
- Deposit results in storage for later use
- Determine successor instruction

Processor Overview

Overall Dataflow


PC fetches instructions

Instructions select operand registers, ALU immediate values

ALU computes values

Load/Store addresses computed in ALU

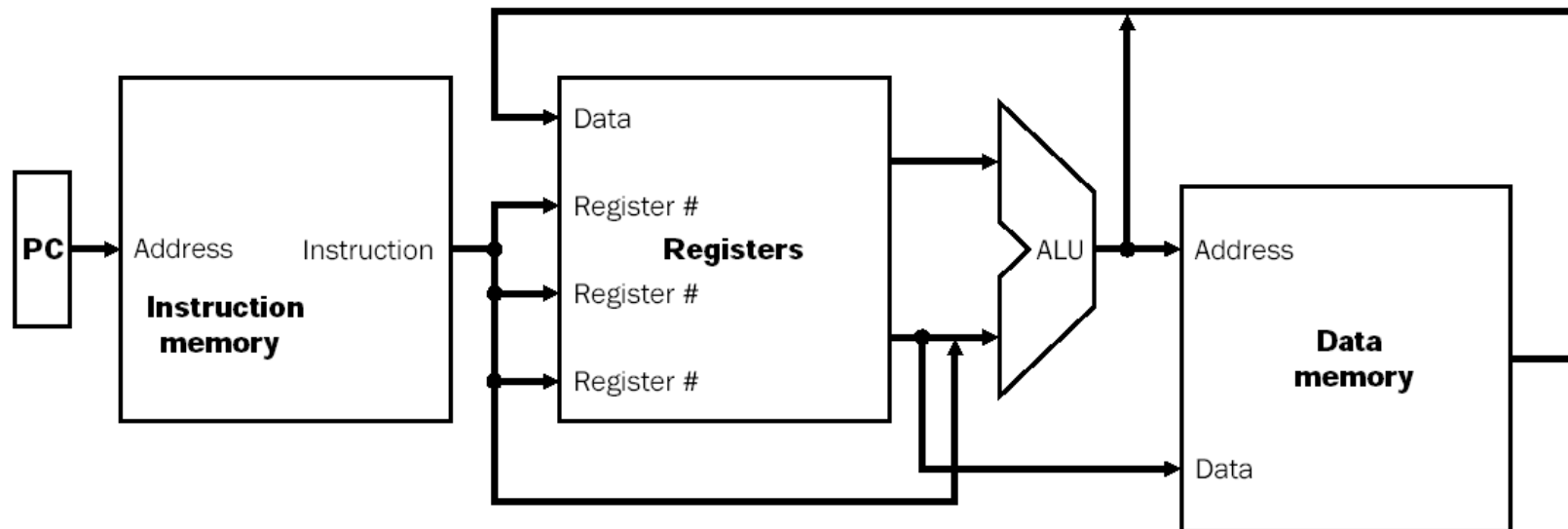Result goes to register file or Data memory



Processor Design

Convert instructions to Register Transfer Level (RTL) specification

```
Instruction ← Memory[PC];
```


```
PC ← PC + 4;
```

RTL specifies required interconnection of units

Control designed to achieve given paths for each instruction

Instruction Fetch
 
```
Instruction = Mem[PC];    // Fetch Instruction  
PC = PC + 4;             // Increment PC (32bit)
```



Add/Subtract RTL

Add instruction: `add rd, rs, rt`

→ `Instruction = Mem[PC];`

`Reg[rd] = Reg[rs] + Reg[rt];`


→ `PC = PC + 4;`

Subtract instruction: `sub rd, rs, rt`

`Instruction = Mem[PC];`



`Reg[rd] = Reg[rs] (-) Reg[rt];`

`PC = PC + 4;`

 

Datapath for Reg/Reg Ops

Reg[rd] ← Reg[rs] op Reg[rt];

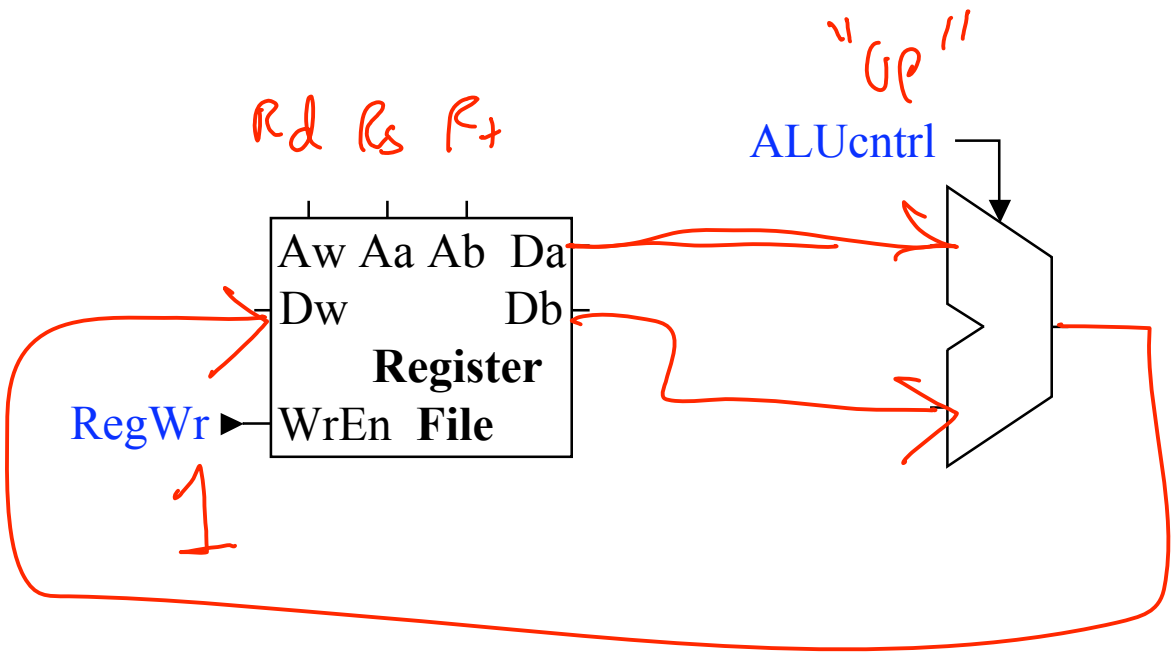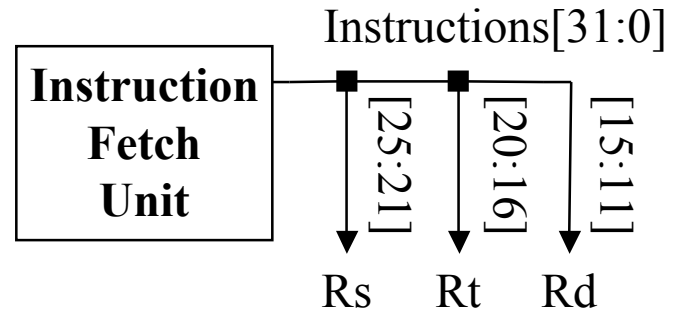


Add Immediate RTL

Add immediate instruction: `addi rt, rs, imm`

→ `Instruction = Mem[PC];`


`Reg[rt] = Reg[rs] + SignExtend(imm);` ←

→ `PC = PC + 4;`

 

Datapath + Immediate Ops
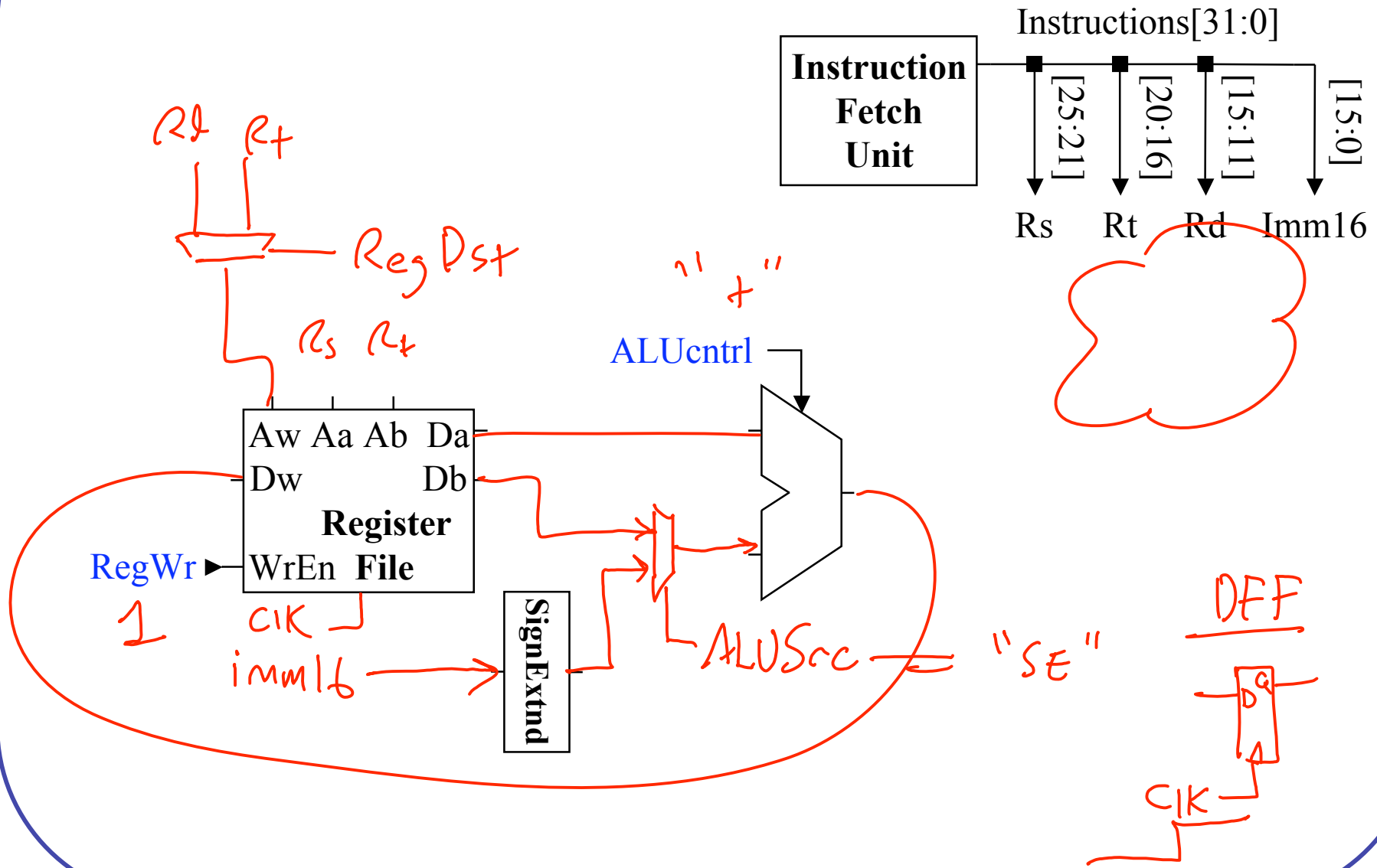
$$\text{Reg}[rt] = \text{Reg}[rs] + \text{SignExtend}(\text{imm});$$



Load RTL


Load Instruction: `lw rt, imm(rs)`

→ `Instruction = Mem[PC];`

`Addr = Reg[rs] + SignExtend(imm);` ←

`Reg[rt] = Mem[Addr];` ←



→ `PC = PC + 4;`

 

Datapath + Load

```

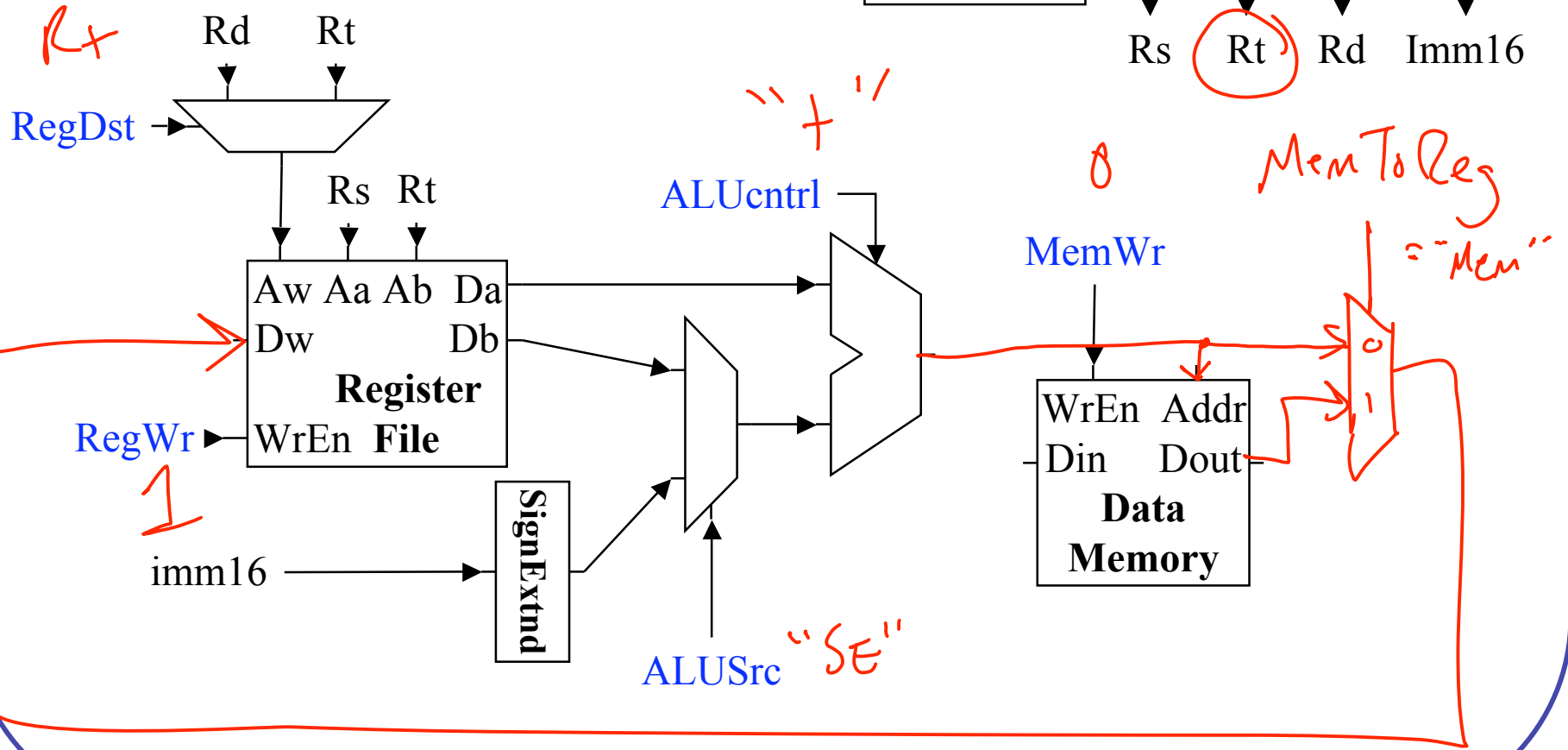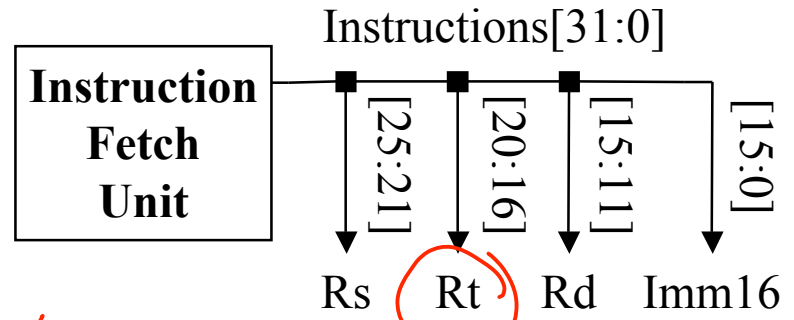Addr = Reg[rs] + SignExtend(imm);
Reg[rt] = Mem[Addr];
    
```



Store RTL


Store Instruction: `sw rt, imm(rs)`

`Instruction = Mem[PC];`

`Addr = Reg[rs] + SignExtend(imm);` ←

`Mem[Addr] = Reg[rt];` ←

`PC = PC + 4;`

 


Datapath + Store

$Addr = Reg[rs] + SignExtend(imm);$

$Mem[Addr] = Reg[rt];$

Note: State of RegWr, MemToReg?

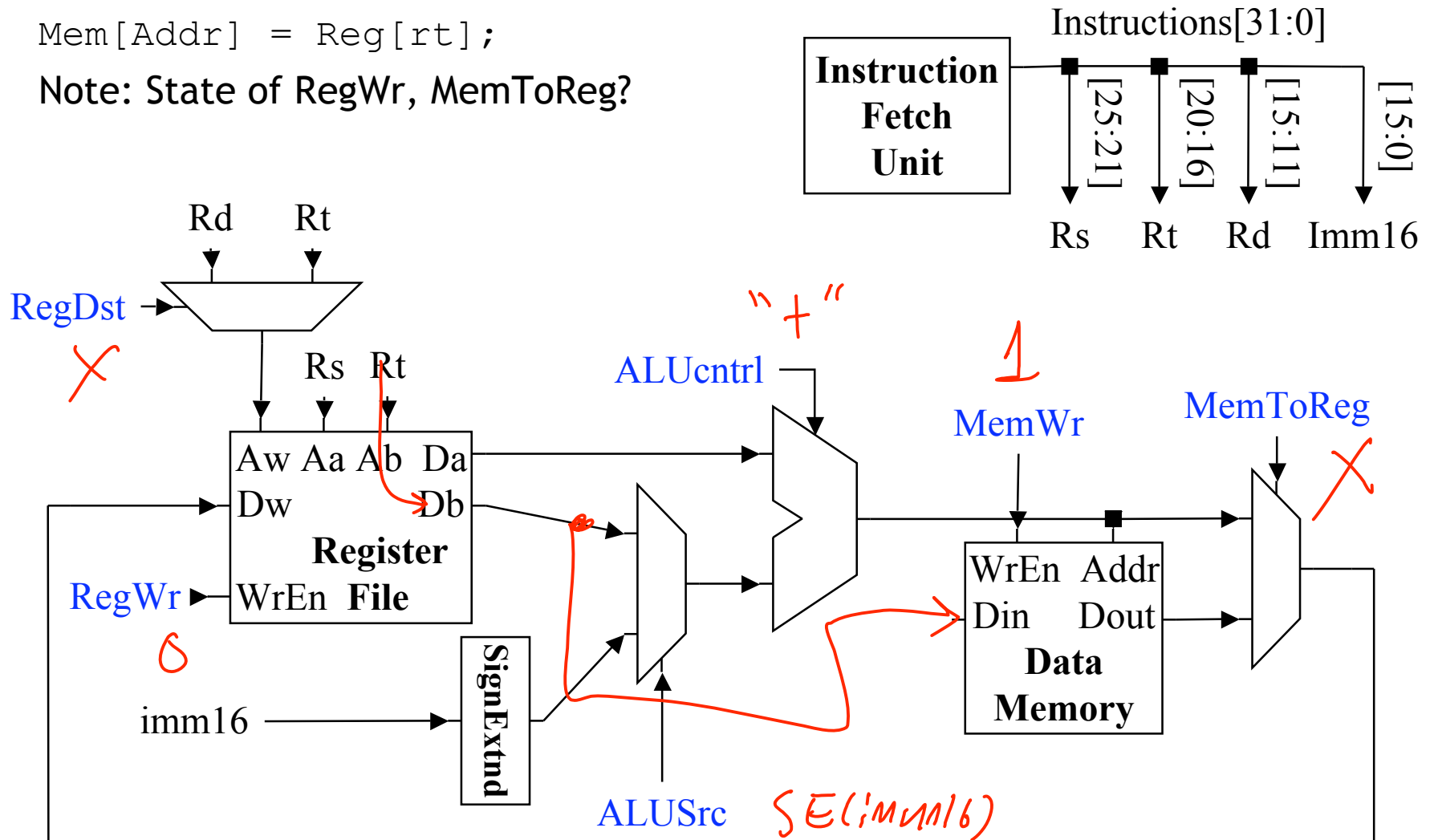

Branch RTL

Branch Instruction: `beq rs, rt, imm`

✓ `Instruction = Mem[PC];`

`Cond = (Reg[rs] - Reg[rt]) == 0; // Test equality`


`if (Cond)`

→ `PC = PC + 4 + SignExtend(imm)*4; // Neg for backward`
`// *4: LSbits == 00`

`else`

→ `PC = PC + 4;`

 
31 30 29 28 27 26 25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 09 08 07 06 05 04 03 02 01 00



Datapath + Branch



```

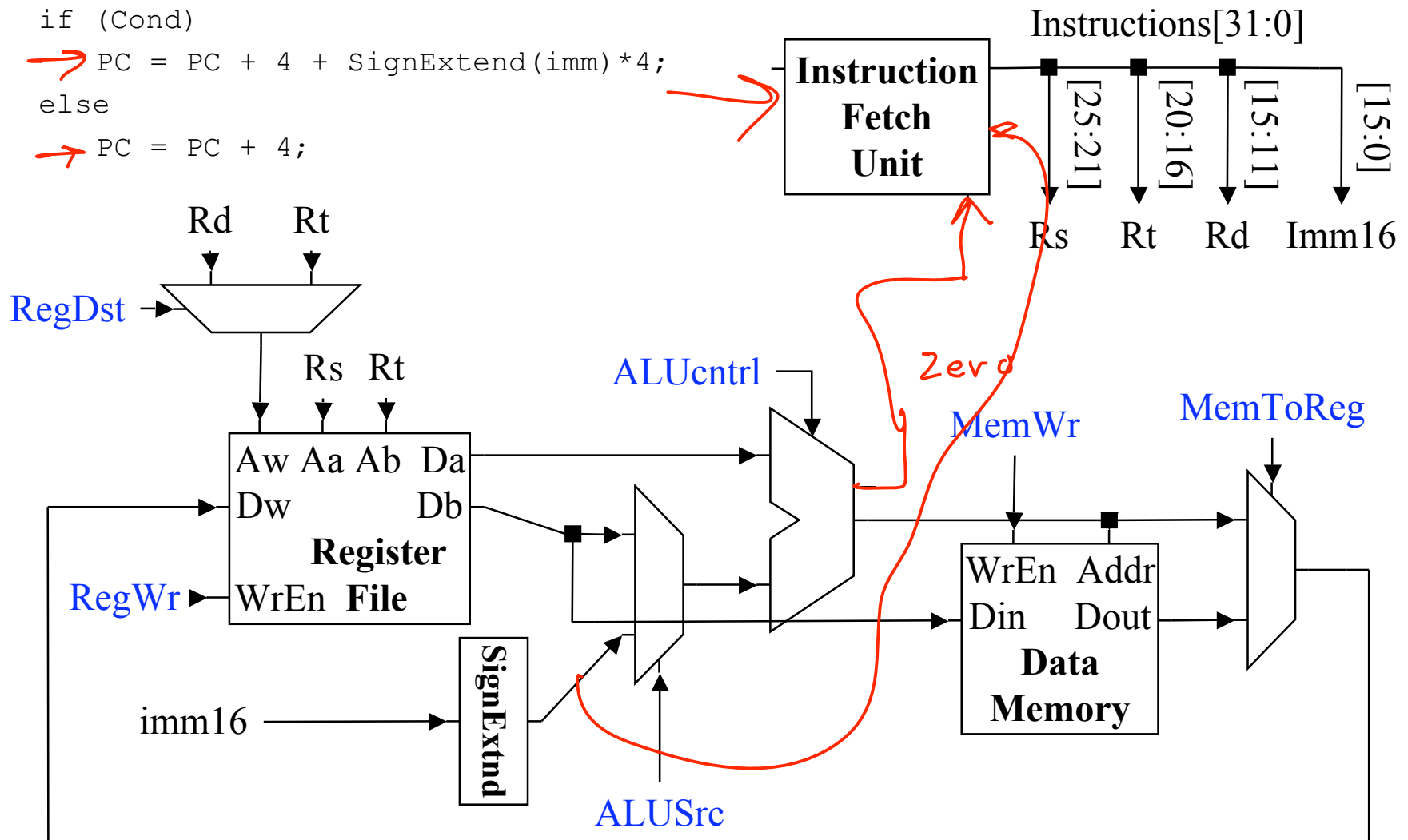Cond = (Reg[rs] - Reg[rt]) == 0;
if (Cond)
    → PC = PC + 4 + SignExtend(imm)*4;
else
    → PC = PC + 4;
    
```



Instruction Fetch + Branch
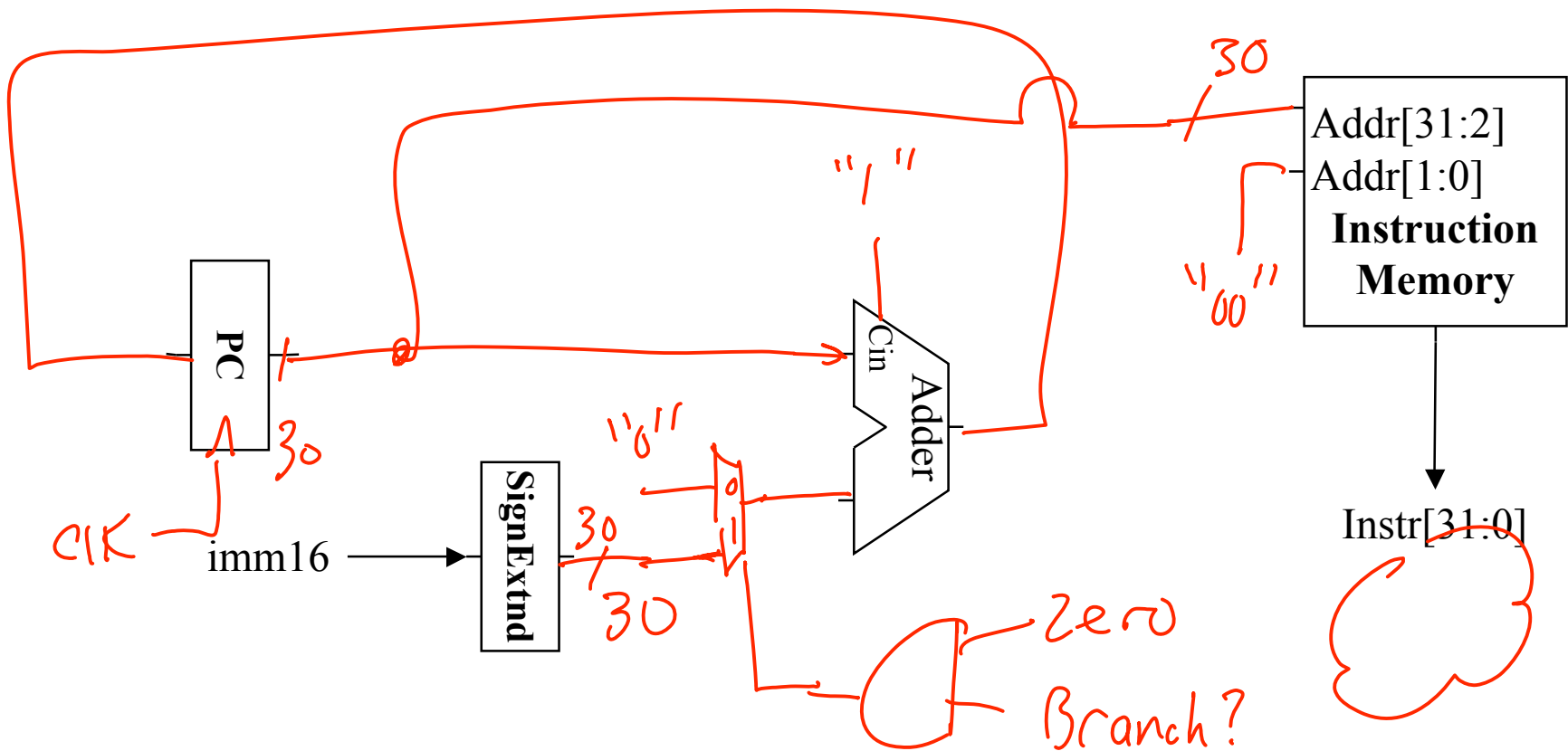 
```
Cond = (Reg[rs] - Reg[rt]) == 0;  
if (Cond)  
    PC = PC + 4 + SignExtend(imm)*4;  
else  
    PC = PC + 4;
```




Jump RTL

Store Instruction: j target


Instruction = Mem[PC];

PC = { PC[31:28], target[25:0], "00" };

 


Instruction Fetch + Jump

PC = { PC[31:28], target[25:0], "00" };

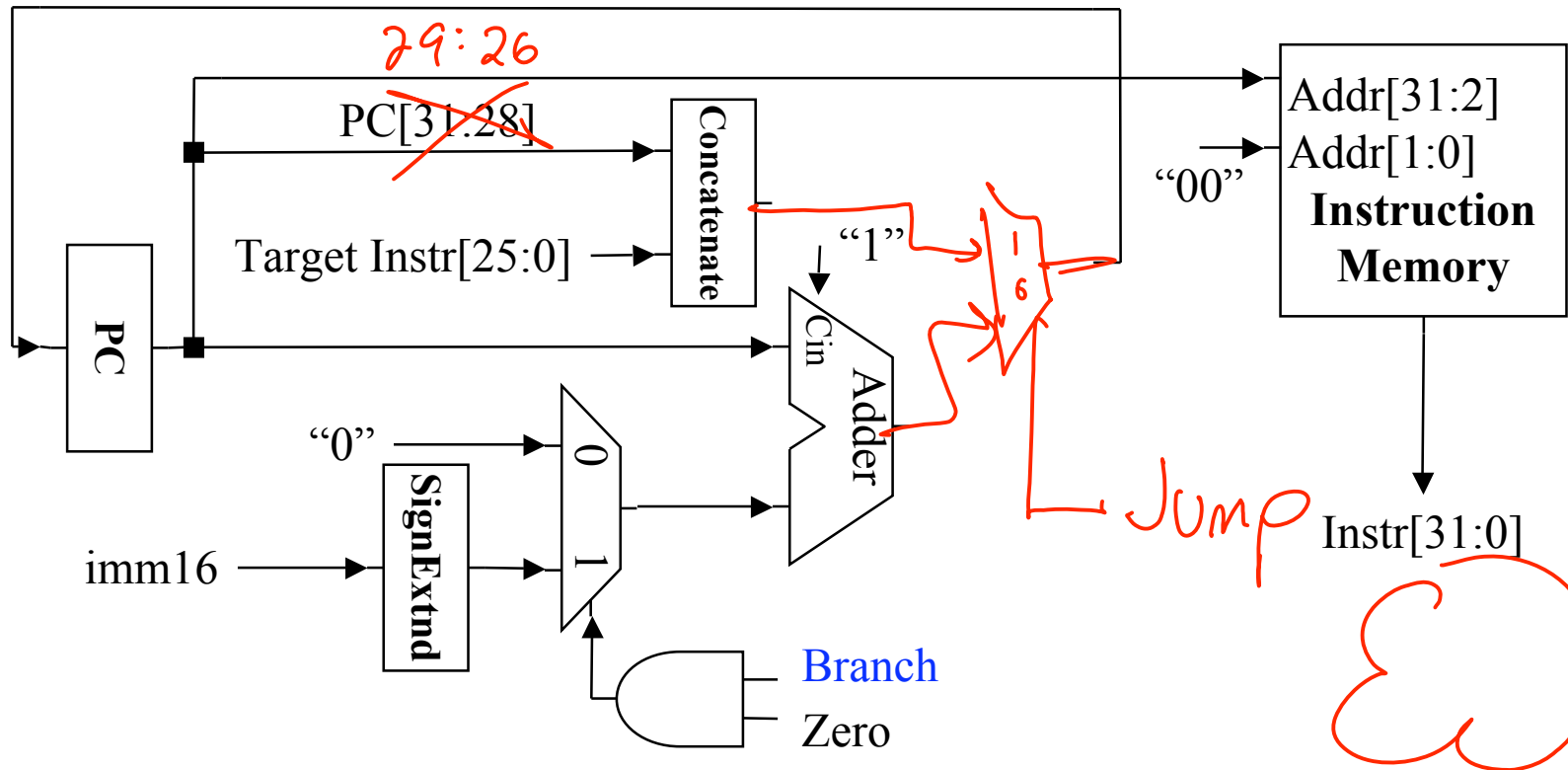


Complete Datapath

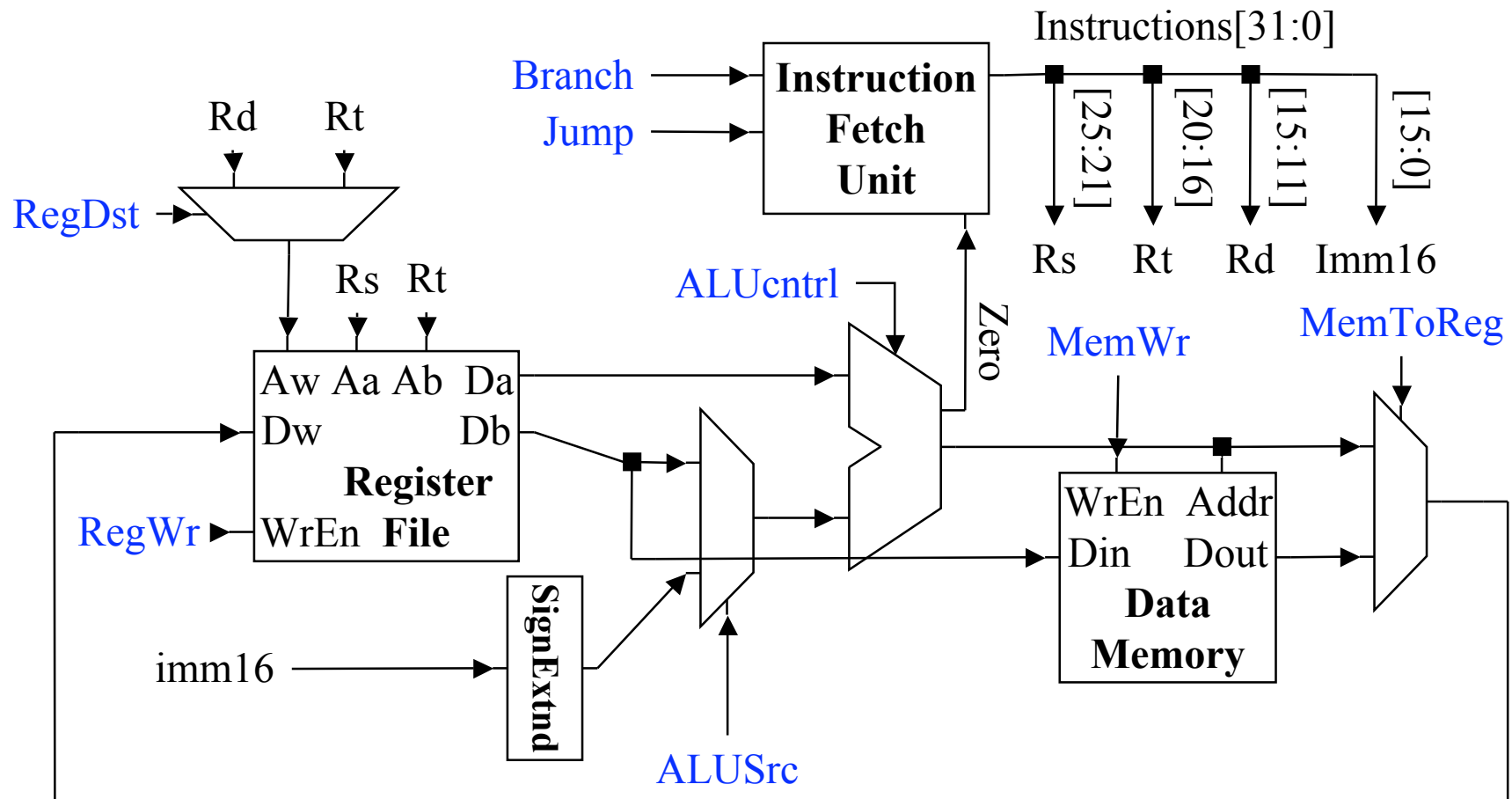


Complete Fetch Unit

FIX

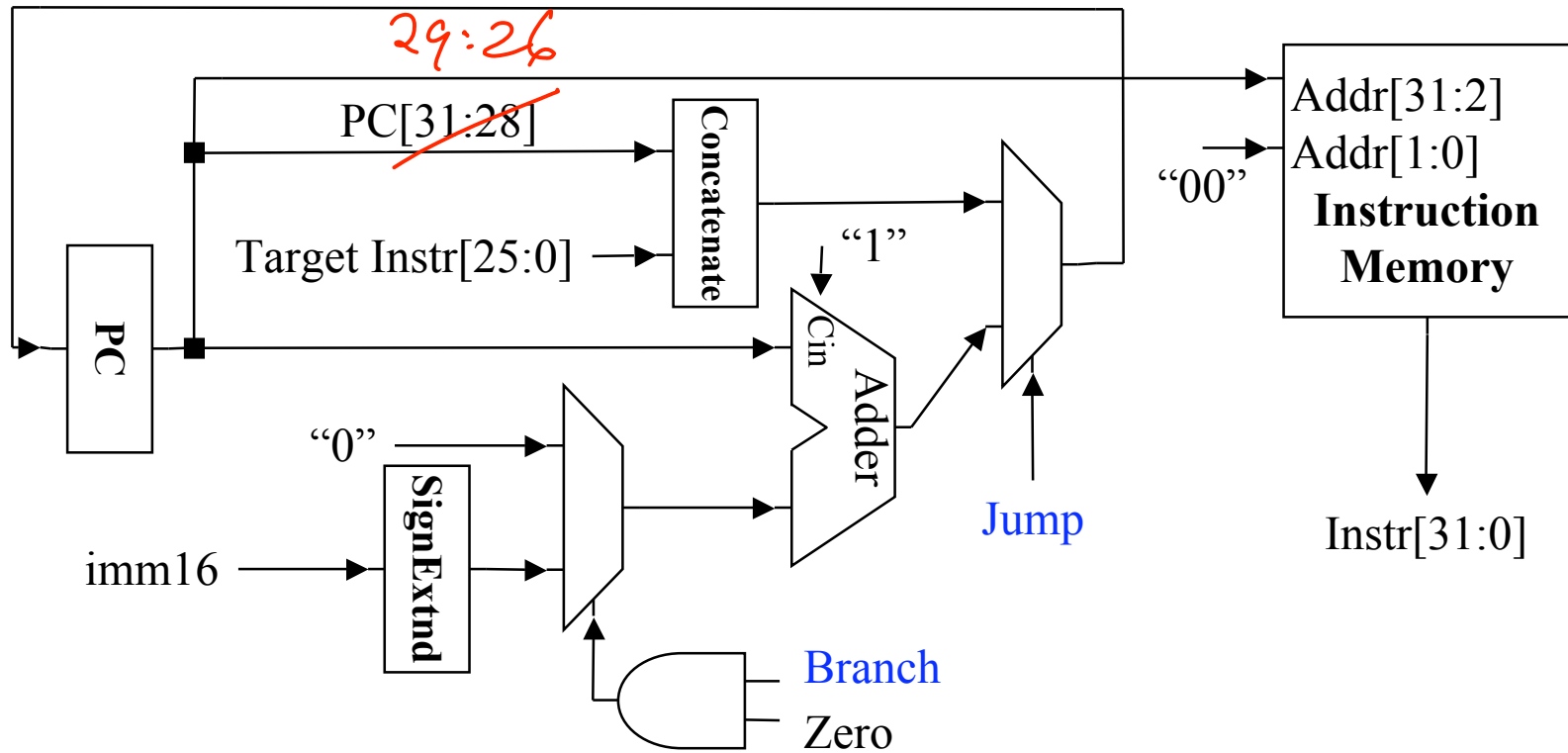

Control

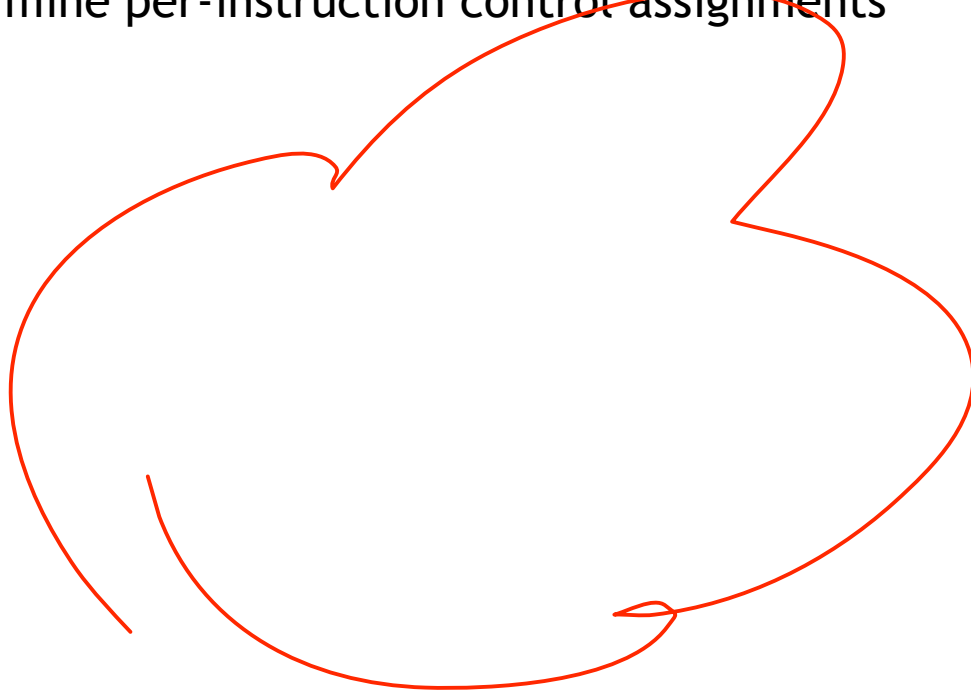- Identify control points for pieces of datapath
 - Instruction Fetch Unit
 - ALU
 - Memories
 - Datapath muxes
 - Etc.
- Use RTL for determine per-instruction control assignments




Control Signals

Func	10000	100010	XXX	XXX	XXX	XXX
Op	000000	000000	100011	101011	000100	000010
	add	sub	lw	sw	beq	j
<i>Reg Dst</i>						

Add Control

```

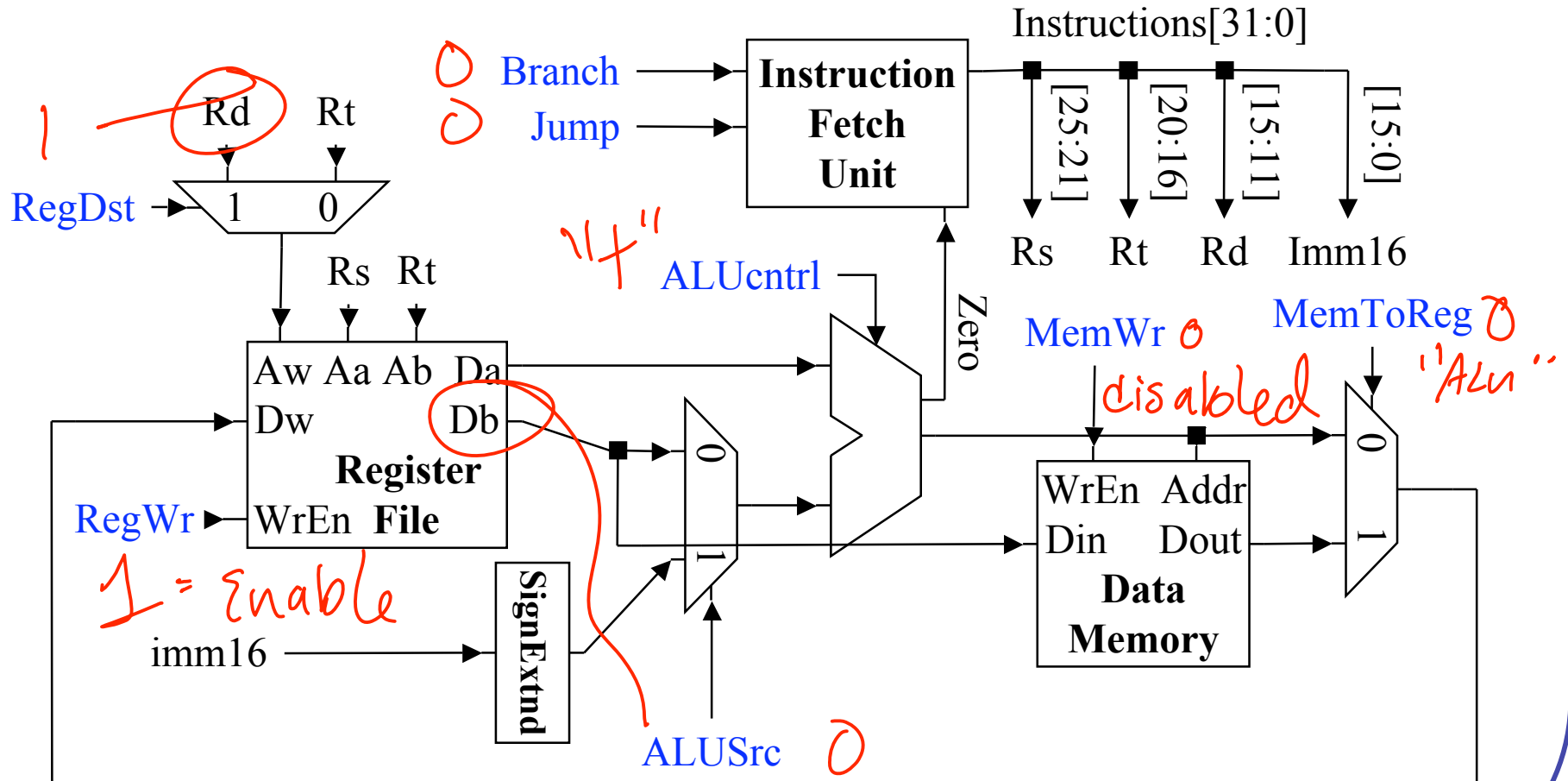add rd, rs, rt
Instruction = Mem[PC];
Reg[rd] = Reg[rs] + Reg[rt];
PC = PC + 4;
    
```



Control Signals


in + out

Func	10000	100010	XXX	XXX	XXX	XXX
Op	000000	000000	100011	101011	000100	000010
	add	sub	lw	sw	beq	j
RegDst	1	1	0	X	X	X
ALUSrc	0	0	1	1	0	X
MemToReg	0	0	1	X	X	X
RegWr	1	1	1	0	0	0
MemWr	0	0	0	1	0	0
Branch	0	0	0	0	1	X
Jump	0	0	0	0	0	1
ALUCntrl	Add	Sub	Add	Add	Sub	X

Subtract Control

```

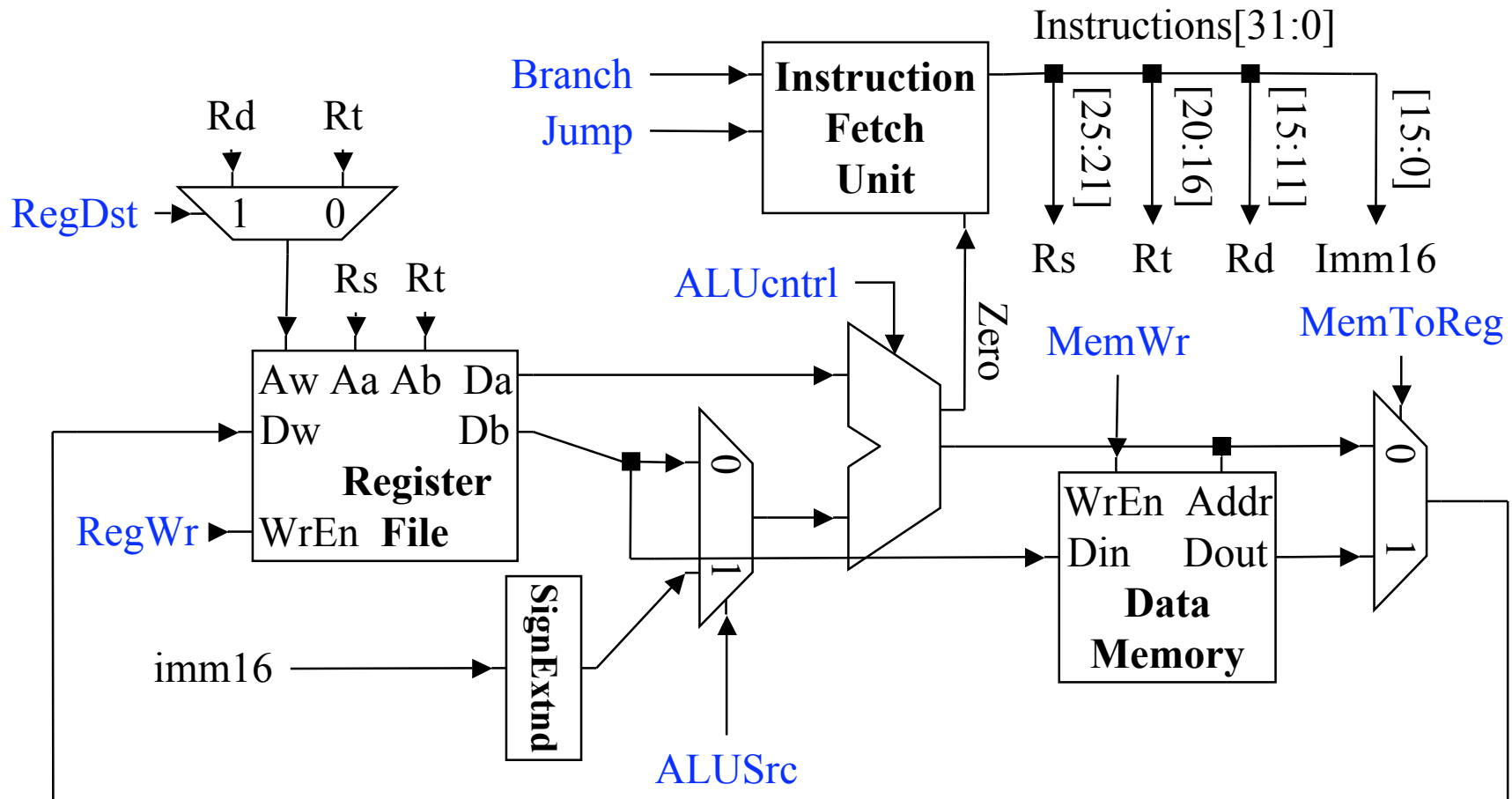
sub rd, rs, rt
Instruction = Mem[PC];
Reg[rd] = Reg[rs] - Reg[rt];
PC = PC + 4;
    
```



Load Control


```

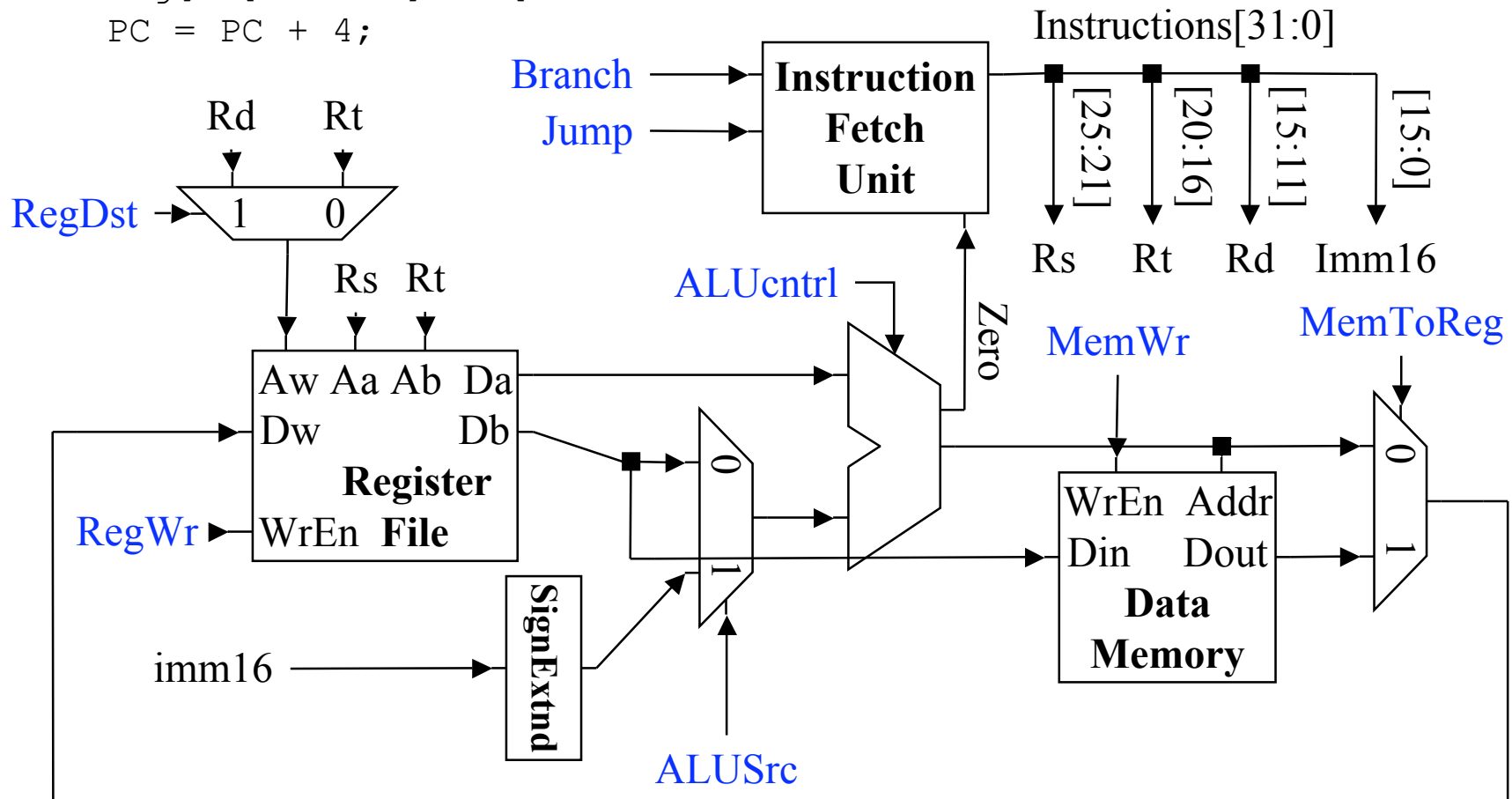lw rt, imm(rs)
Instruction = Mem[PC];
Addr = Reg[rs] + SignExtend(imm);
Reg[rt] = Mem[Addr];
PC = PC + 4;
    
```



Store Control

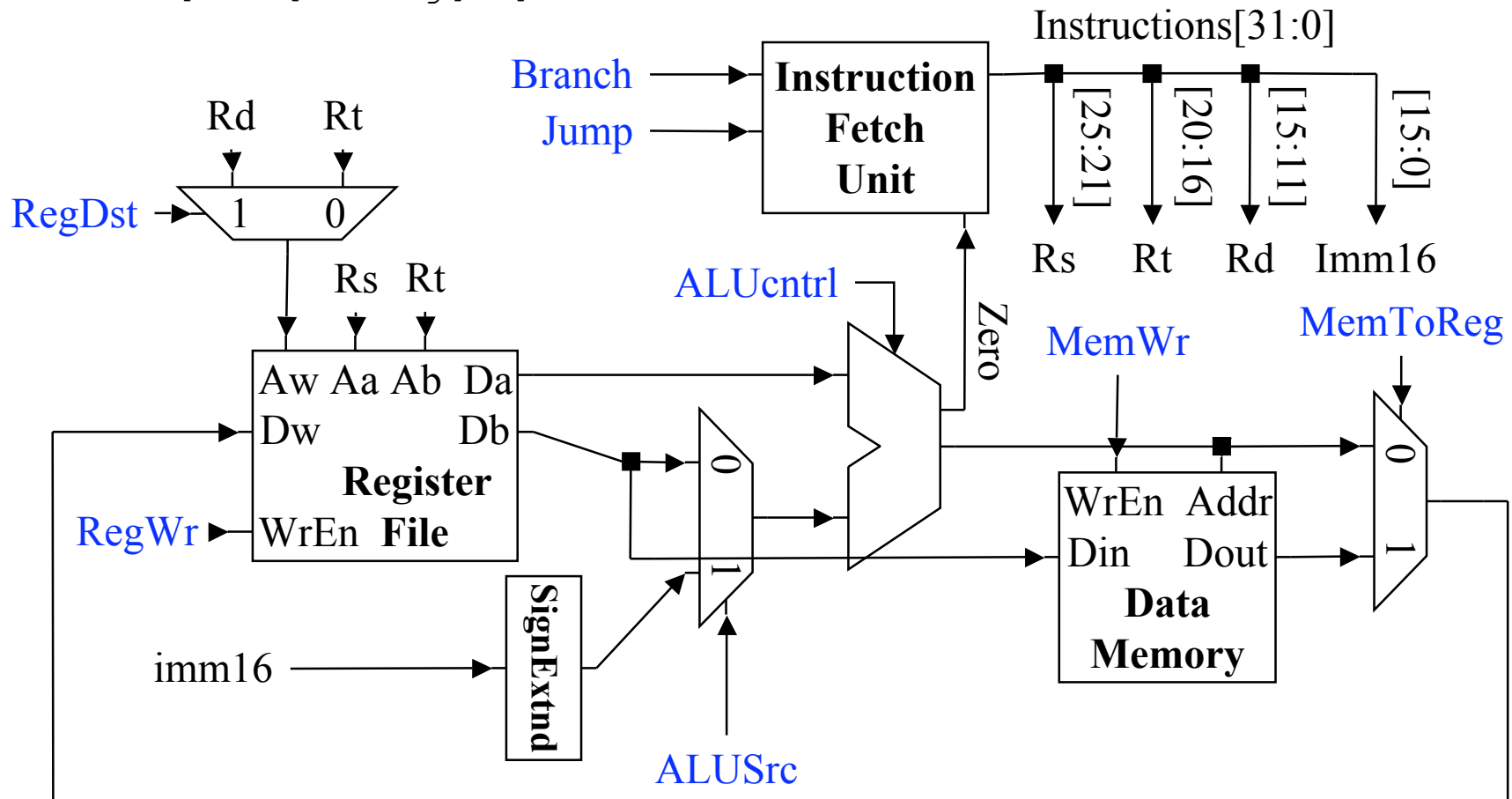
```
sw rt, imm(rs)
Instruction = Mem[PC];
Addr = Reg[rs] + SignExtend(imm);
Mem[Addr] = Reg[rt];
```



Branch Control


```

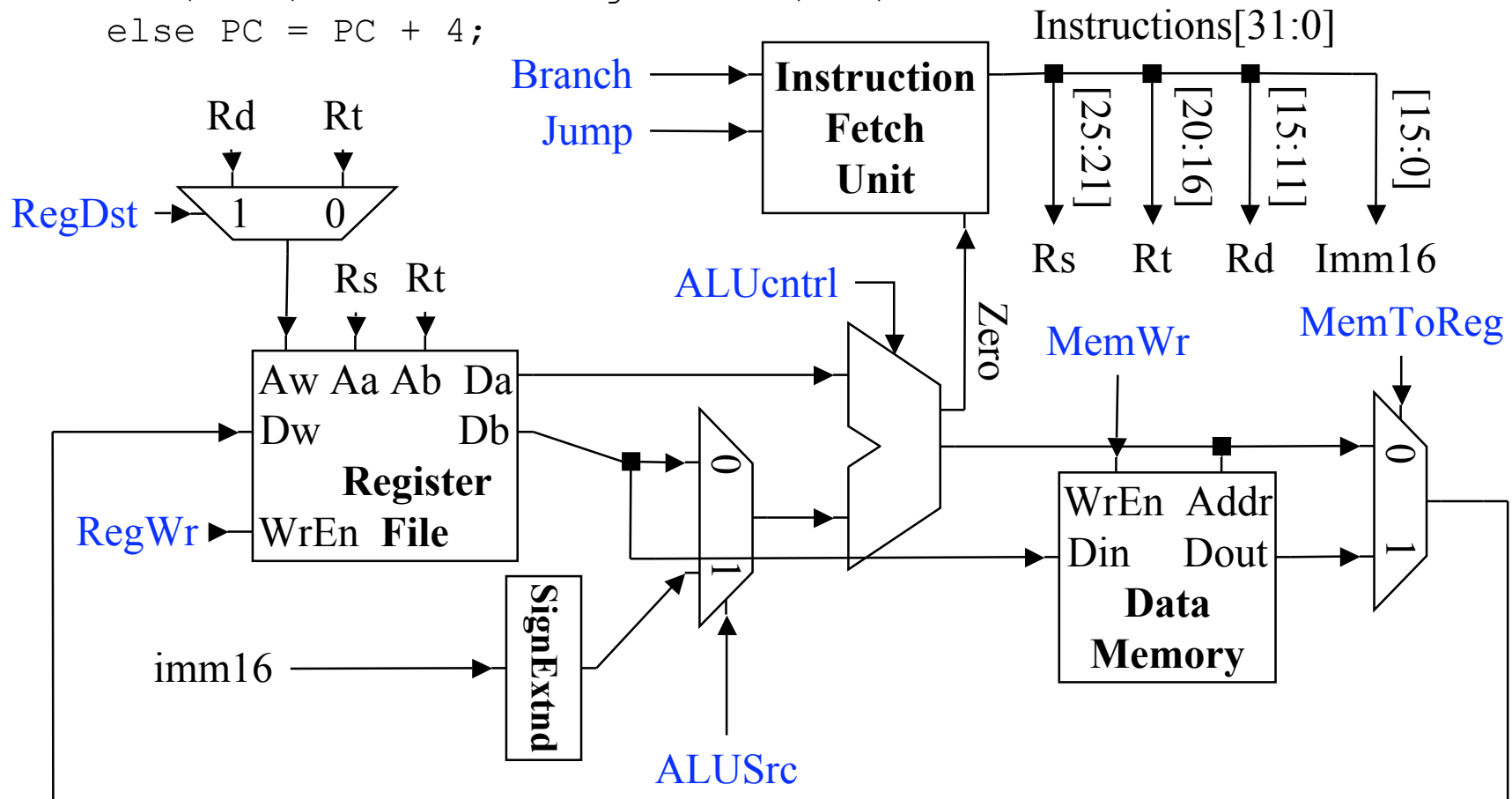beq rs, rt, imm
Instruction = Mem[PC];
Cond = (Reg[rs] - Reg[rt]) == 0;
if (Cond) PC = PC+4+SignExtend(imm)*4;
else PC = PC + 4;
    
```



Branch Control (cont.)

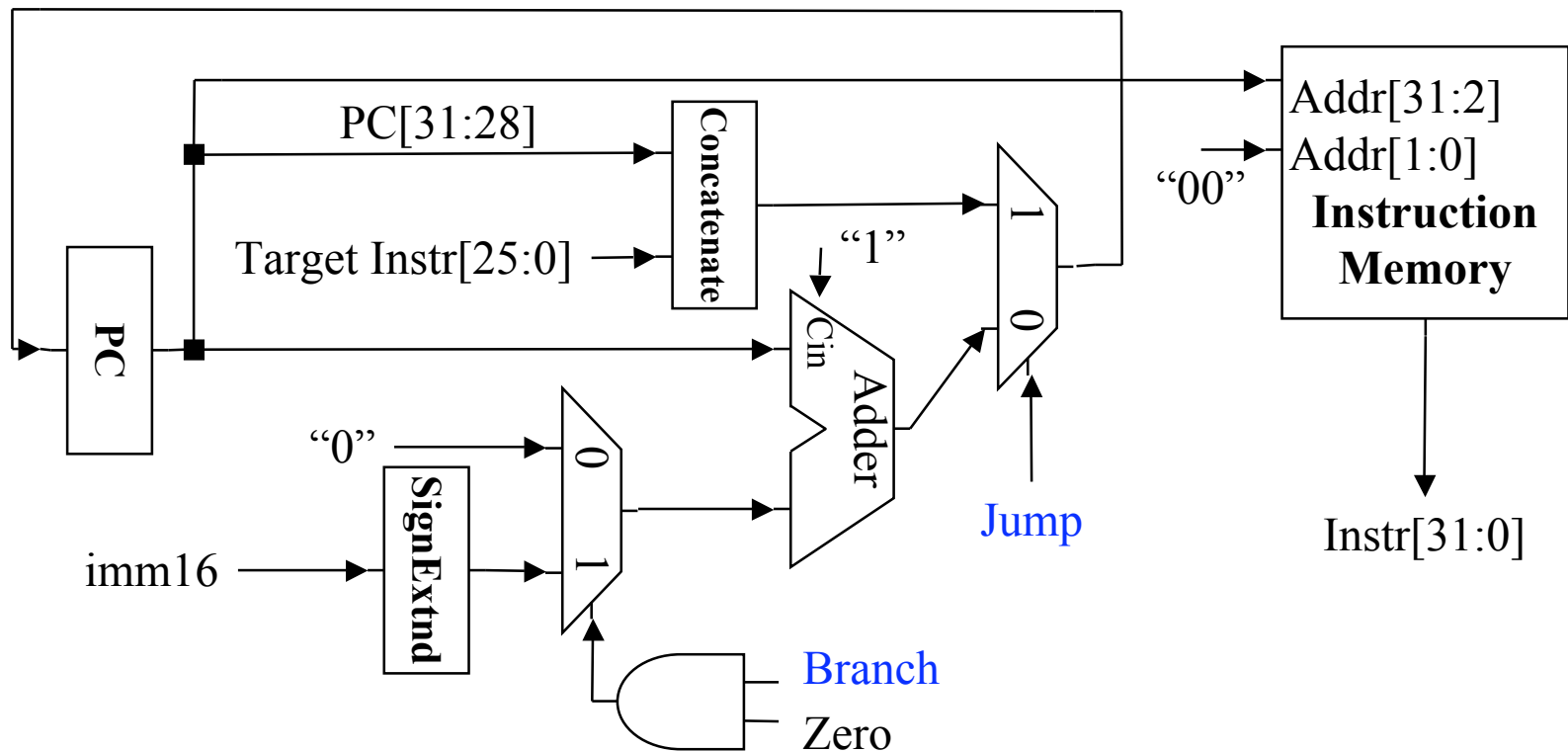
```
beq rs, rt, imm
Instruction = Mem[PC];
Cond = (Reg[rs] - Reg[rt]) == 0;
if (Cond) PC = PC+4+SignExtend(imm)*4;
else PC = PC + 4;
```



Jump Control

```

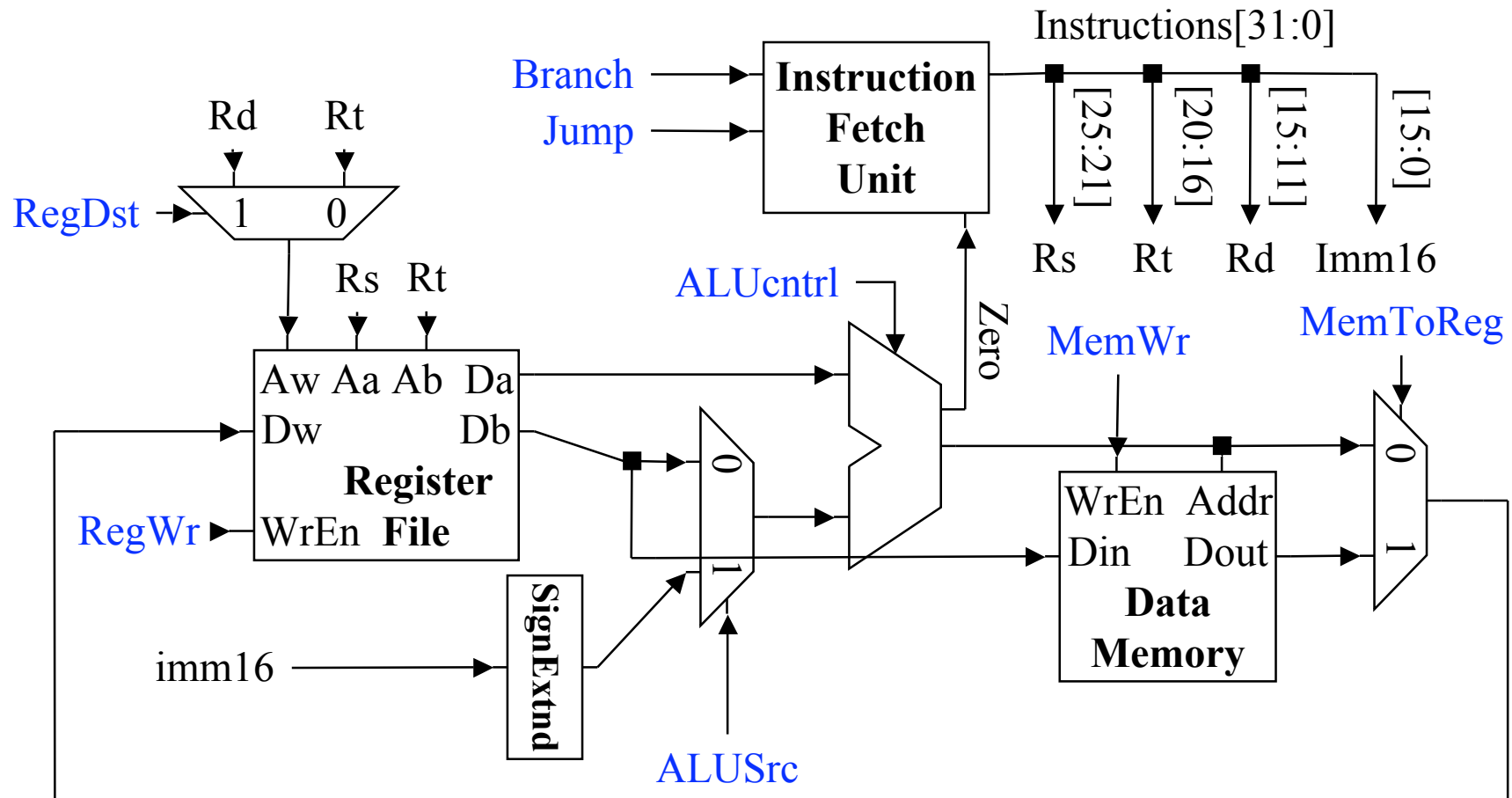j target
Instruction = Mem[PC];
PC = { PC[31:28], target[25:0], "00" };
    
```



Jump Control (cont.)

```
j target  
Instruction = Mem[PC];  
PC = { PC[31:28], target[25:0], "00" };
```

